

## **Unit 4. Application of Boolean Algebra Minterm and Maxterm Expansions**

Spring 2015

School of Electrical Engineering

Prof. Jong-Myon Kim

# Objectives – To Learn

---

## Topics introduced in this chapter

- ⇒ Conversion of English Sentences to Boolean Equations
- ⇒ Combinational Logic Design Using a Truth Table
- ⇒ Minterm and Maxterm Expansions
- ⇒ General Minterm and Maxterm Expansions
- ⇒ Incompletely Specified Functions (Don't care term)
- ⇒ Examples of Truth Table Construction
- ⇒ Design of Binary Adders (Full Adder) and Subtractors

# Conversion of English Sentences to Boolean Eq.

---

## Steps in designing a single-output combinational switching circuit

- ⇒ Find switching function which specifies the desired behavior of the circuit
- ⇒ Find a simplified algebraic expression for the function
- ⇒ Realize the simplified function using available logic elements

1. F is 'true' if A and B are both 'true'  $\rightarrow F=AB$


# Conversion of English Sentences to Boolean Eq.

1. The alarm will ring( $Z$ ) iff the alarm switch is turned on( $A$ ) **and** the door is not closed( $B'$ ), **or** it is after 6PM( $C$ ) and window is not closed( $D'$ )

2. Boolean Equation


$$Z = AB' + CD'$$

3. Circuit realization

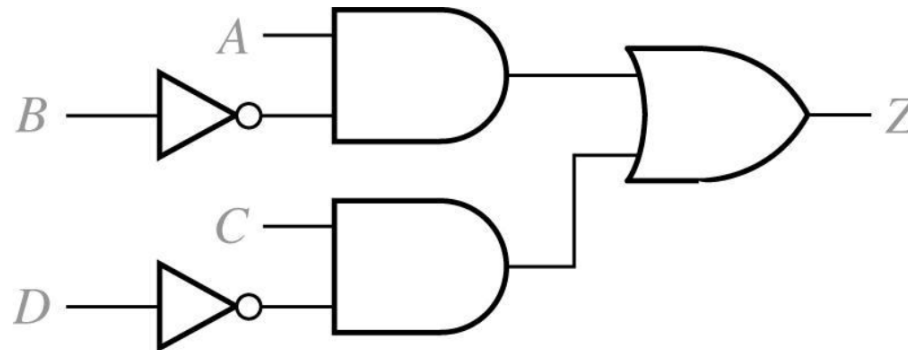

# Combinational Logic Design Using a Truth Table
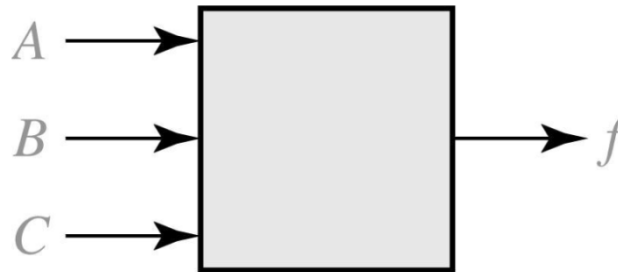
## - Combinational Circuit with Truth Table



(a)

$A$	$B$	$C$	$f$	$f'$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)

When expression for  $f=1 \rightarrow$

$$f = A'BC + ABC' + ABC + ABC + ABC$$

# Combinational Logic Design Using a Truth Table


Original equation →

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

Simplified equation →


$$f = A'BC + AB' + AB = A'BC + A = A + BC$$

Circuit realization →

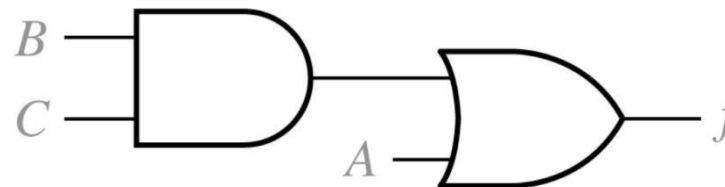

# Combinational Logic Design Using a Truth Table
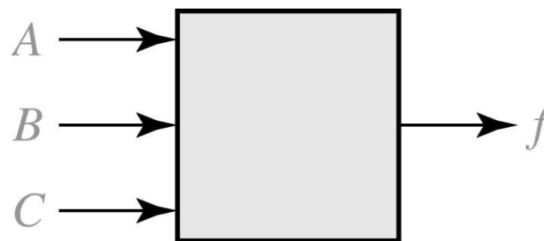
## - Combinational Circuit with Truth Table



(a)

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

(b)

When expression for  $f=0 \rightarrow$

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

$$f = (A + B)(A + B' + C) = A + BC$$

When expression for  $f'=1 \rightarrow$   
and take the complement of  $f$

$$f' = A'B'C' + A'B'C + A'BC'$$

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

# Minterm and Maxterm Expansions

- *Minterm* of  $n$  variables is a product of  $n$  literals in which each variable appears exactly once in either true ( $A$ ) or complemented form ( $A'$ ), but not both. ( $\rightarrow m_0$ )

-Minterm expansion,

-Standard Sum of Product  $\rightarrow$

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

$$f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$f(A, B, C) = \sum m(3, 4, 5, 6, 7)$$

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A' B' C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A' B' C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A' B C' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A' B C = m_3$	$A + B' + C' = M_3$
4	1 0 0	$A B' C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$A B' C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$A B C' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$A B C = m_7$	$A' + B' + C' = M_7$



# Minterm and Maxterm Expansions

---

- *Maxterm* of  $n$  variables is a sum of  $n$  literals in which each variable appears exactly once in either true ( $A$ ) or complemented form ( $A'$ ), but not both. ( $\rightarrow M_0$ )


- Maxterm expansion,
- Standard Product of Sum  $\rightarrow$

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

$$f(A, B, C) = M_0 M_1 M_2$$

$$f(A, B, C) = \prod M(0, 1, 2)$$

# Minterm and Maxterm Expansions
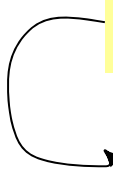
$$f(A, B, C) = m_3 + m_4 + m_5 + m_6 + m_7$$

$$f' = m_0 + m_1 + m_2 = \sum m(0,1,2)$$

$$f(A, B, C) = M_0 M_1 M_2 \longrightarrow f' = \prod M(3,4,5,6,7) = M_3 M_4 M_5 M_6 M_7$$

- *Minterm* and *Maxterm* expansions are complement each other

$$f' = (m_3 + m_4 + m_5 + m_6 + m_7)' = m'_3 m'_4 m'_5 m'_6 m'_7 = M_3 M_4 M_5 M_6 M_7$$

$$f' = (M_0 M_1 M_2)' = M'_0 + M'_1 + M'_2 = m_0 + m_1 + m_2$$

P89 Example

# General Minterm and Maxterm Expansions

A B C	F
0 0 0	$a_0$
0 0 1	$a_1$
0 1 0	$a_2$
0 1 1	$a_3$
1 0 0	$a_4$
1 0 1	$a_5$
1 1 0	$a_6$
1 1 1	$a_7$

-General truth table  
for 3 variables  
-  $a_i$  is either '0' or '1'

- Minterm expansion for general function

$$F = a_0m_0 + a_1m_1 + a_2m_2 + \dots + a_7m_7 = \sum_{i=0}^7 a_i m_i$$

$a_i=1$ , minterm  $m_i$  is present

$a_i=0$ , minterm  $m_i$  is not present

- Maxterm expansion for general function

$$F = (a_0 + M_0)(a_1 + M_1)(a_2 + M_2) \dots (a_7 + M_7) = \prod_{i=0}^7 (a_i + M_i)$$

$a_i=1$ ,  $a_i + M_i=1$ , Maxterm  $M_i$  is not present

$a_i=0$ , Maxterm is present

# General Minterm and Maxterm Expansions

$$F' = \left[ \prod_{i=0}^7 (a_i + M_i) \right]' = \sum_{i=0}^7 a'_i M'_i = \sum_{i=0}^7 a'_i m_i$$

→ All minterm which are not present in  $F$  are present in  $F'$

$$F' = \left[ \sum_{i=0}^7 a_i m_i \right]' = \prod_{i=0}^7 (a'_i + m'_i) = \prod_{i=0}^7 (a'_i + M_i)$$

→ All maxterm which are not present in  $F$  are present in  $F'$

$$F = \sum_{i=0}^{2^n-1} a_i m_i = \prod_{i=0}^{2^n-1} (a_i + M_i)$$
$$F' = \sum_{i=0}^{2^n-1} a'_i m_i = \prod_{i=0}^{2^n-1} (a'_i + M_i)$$

# General Minterm and Maxterm Expansions

*If  $i$  and  $j$  are different,  $m_i m_j = 0$*

$$f_1 = \sum_{i=0}^{2^n-1} a_i m_i \qquad f_2 = \sum_{j=0}^{2^n-1} b_j m_j$$

$$f_1 f_2 = \left( \sum_{i=0}^{2^n-1} a_i m_i \right) \left( \sum_{j=0}^{2^n-1} b_j m_j \right) = \sum_{i=0}^{2^n-1} \sum_{j=0}^{2^n-1} a_i b_j m_i m_j = \sum_{i=0}^{2^n-1} a_i b_i m_i$$

**Example**


$$f_1 = \sum m(0,2,3,5,9,11) \text{ and } f_2 = \sum m(0,3,9,11,13,14)$$

$$f_1 f_2 = \sum m(0,3,9,11)$$

# Conversion between Minterm and Maxterm Expansions of F and F'

	Minterm Expansion of f	Maxterm Expansion of f	Minterm Expansion of f'	Maxterm Expansion of f'
$f = \sum m(3,4,5,6,7)$		$\prod M(0,1,2)$	$\sum m(0,1,2)$	$\prod M(3,4,5,6,7)$
$f = \prod M(0,1,2)$	$\sum m(3,4,5,6,7)$		$\sum m(0,1,2)$	$\prod M(3,4,5,6,7)$

# Incompletely Specified Functions

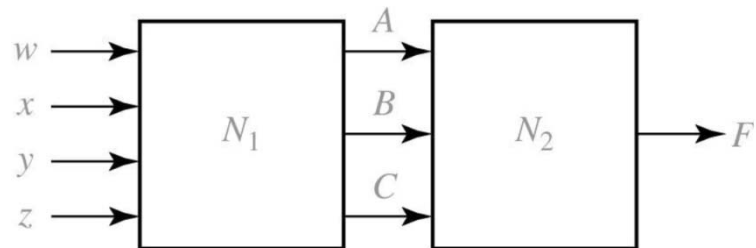

If  $N_1$  output does not generate all possible combination of A,B,C, the output of  $N_2(F)$  has 'don't care' values.

Truth Table with Don't Cares

A	B	C	F
0	0	0	1
0	0	1	X
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	X
1	1	1	1

# Incompletely Specified Functions

Finding Function:

Case 1: assign '0' on X's

$$F = A'B'C' + A'BC + ABC = A'B'C' + BC$$

Case 2: assign '1' to the first X and '0' to the second 'X'

$$F = A'B'C' + A'B'C + A'BC + ABC = A'B' + BC$$

Case 3: assign '1' on X's

$$F = A'B'C' + A'B'C + A'BC + ABC' + ABC = A'B' + BC + AB$$

→ The case 2 leads to the simplest function



# Incompletely Specified Functions

- Minterm expansion for incompletely specified function

$$F = \sum m(0,3,7) + \sum d(1,6)$$

Don't Cares

- Maxterm expansion for incompletely specified function


$$F = \prod M(2,4,5) \prod D(1,6)$$

A B C	F
0 0 0	1
0 0 1	X
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	X
1 1 1	1

# Examples of Truth Table Construction

## Example 1 : Binary Adder

a	b	Sum	
0	0	0 0	0+0=0
0	1	0 1	0+1=1
1	0	0 1	1+0=1
1	1	1 0	1+1=2

 


A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$X = AB, Y = A'B + AB' = A \oplus B$$


# Design of Binary Adders and Subtractors
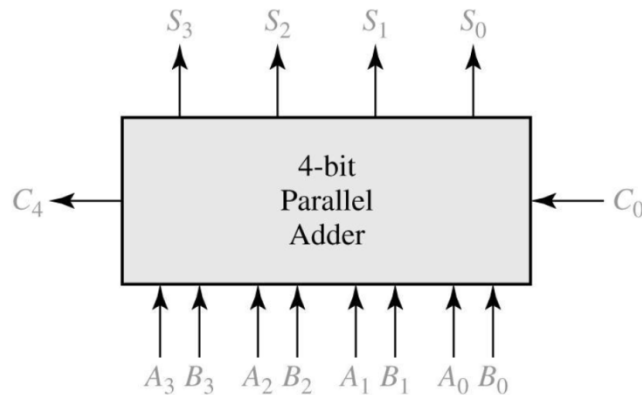
## Parallel Adder for 4 bit Binary Numbers




$$\begin{array}{r} 10110 \text{ (carries)} \\ 1011 \\ +1011 \\ \hline 10110 \end{array}$$

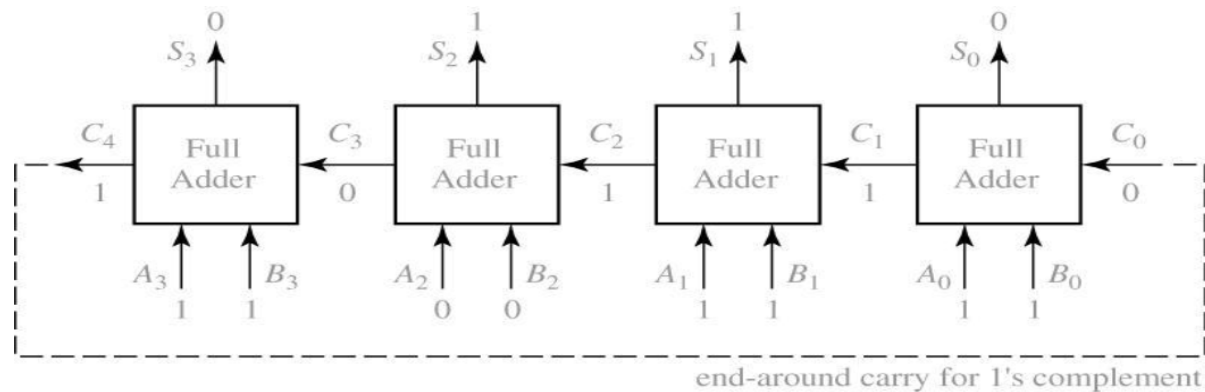Parallel adder composed of four full adders ← Carry Ripple Adder (slow!)


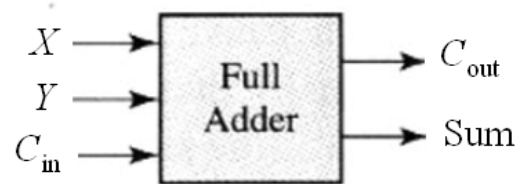
# Design of Binary Adders and Subtractors




Truth Table for a Full

X	Y	C <sub>in</sub>	C <sub>out</sub>	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$\begin{aligned}
 Sum &= X'Y'C_{in} + X'YC'_{in} + XY'C'_{in} + XYC_{in} \\
 &= X'(Y'C_{in} + YC'_{in}) + X(Y'C'_{in} + YC_{in}) \\
 &= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' = X \oplus Y \oplus C_{in}
 \end{aligned}$$
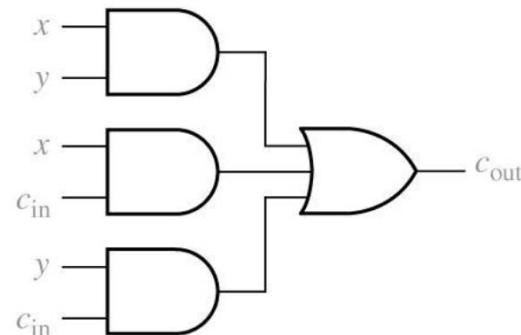
$$\begin{aligned}
 C_{out} &= X'YC_{in} + XY'C_{in} + XYC'_{in} + XYC_{in} \\
 &= (X'YC_{in} + XYC_{in}) + (XY'C_{in} + XYC'_{in}) + (XYC'_{in} + XYC_{in}) \\
 &= YC_{in} + XC_{in} + XY
 \end{aligned}$$


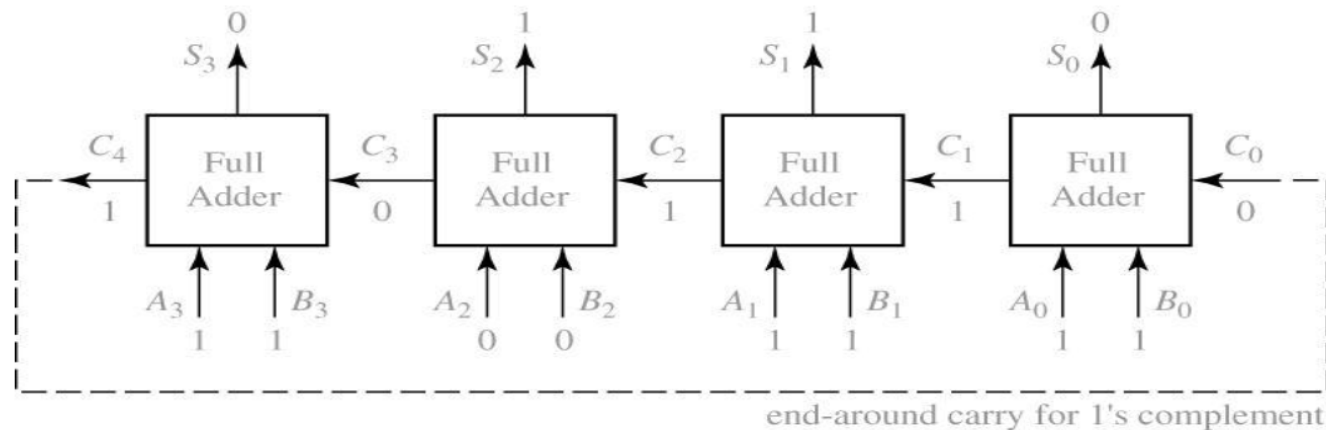
# Design of Binary Adders and Subtractors

When 1's complement is used, the end-around carry is accomplished by connecting C4 to C0 input.



Overflow(V) when adding two signed binary number


$$V = A'_3 B'_3 S_3 + A_3 B_3 S'_3$$

# Subtractors


## Binary Subtractor using full adder

-Subtraction is done by adding the 2's complemented number to be subtracted

-Example:  $A - B$

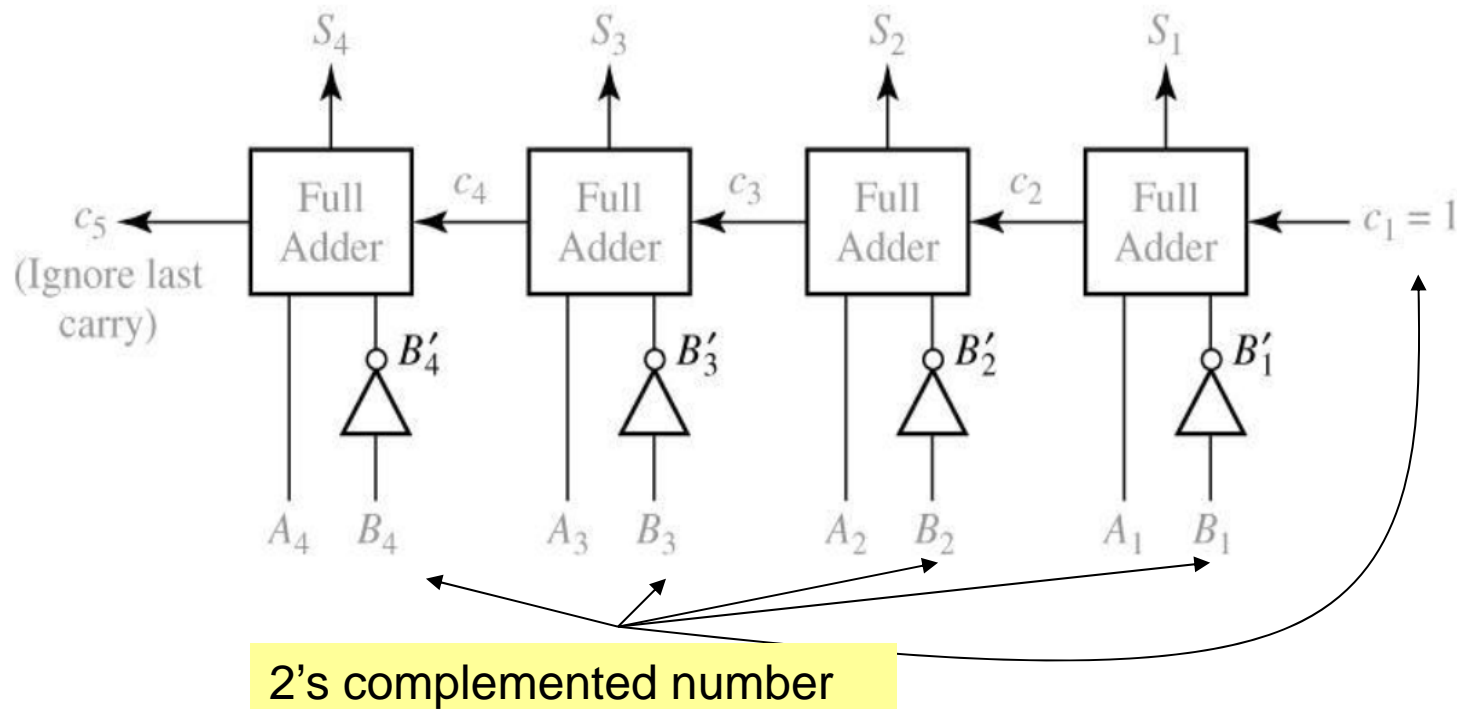
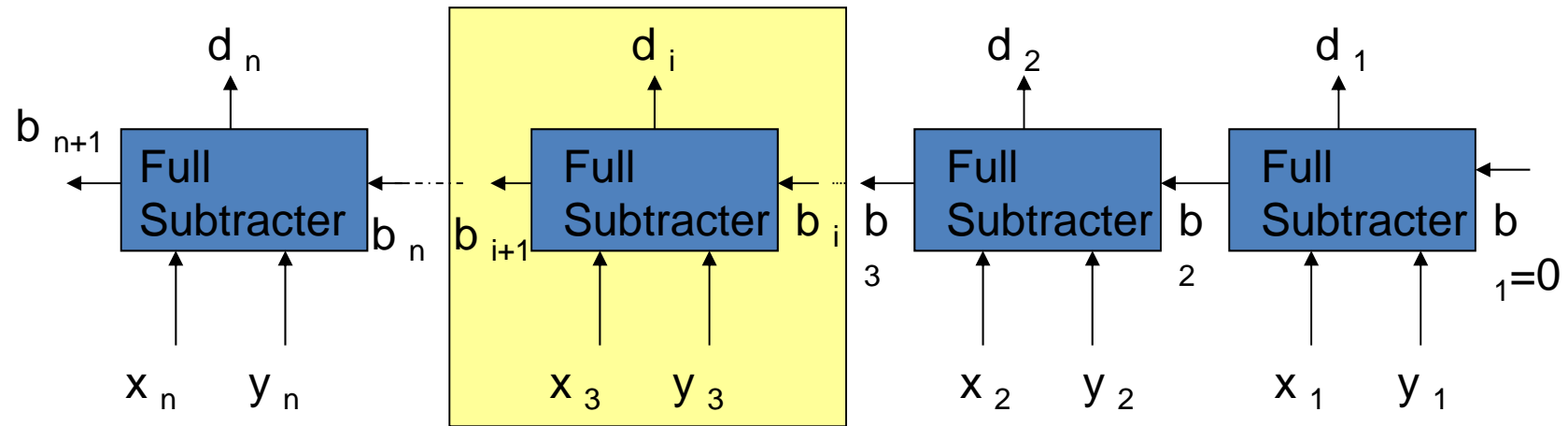
# Parallel Subtractors using Full Subtractor



Truth Table for a Full Subtractor

$x_i$	$y_i$	$b_i$	$b_{i+1}$	$d_i$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1