

Unit 12. Registers & Counters

Spring 2015

School of Electrical Engineering

Prof. Jong-Myon Kim

Objectives – To Learn

1. Explain the operation of registers. Understand how to transfer data between registers using tri-state bus.
2. Explain the shift register operation, how to build them and analyze operation. Construct a timing diagram for a shift register.
3. Explain the operation of binary counters, how to build them using F/F and gates and analyze operation.
4. Given the present state and desired next state of F/F, determine the required F/F inputs.
5. Given the desired counting sequence for a counter, derive F/F input equations.
6. Explain the procedures used for deriving F/F input equation.
7. Construct a timing diagram for a counter by tracing signals through the circuit.

Counters

◆ Counters

- ❖ Simplest sequential networks
- ❖ usually constructed from 2 or more F/F's

◆ Synchronous counter


- ❖ operation of F/F's are synchronized by common input pulse

◆ Asynchronous counter

- ❖ example : ripple counter – the state change of current F/F affects the next F/F

Sync Binary Counter using T F/F

- ◆ Design a binary counter using 3 T F/F's to count clock pulses
- ◆ Counting sequence:
 - ❖ CBA : 000, 001, 010, 011, 100, 101, 110, 111, 000
- ◆ 1. Design a counter by inspection of the counting sequence
- ◆ Observe :
 - ❖ A changes state every time a pulse is received
 - ❖ B changes state every time a pulse is received only if A=1
 - ❖ C changes state every time a pulse is received only if B=A=1
- ◆ solution as in Fig 12-13
- ◆ Verify the operation by tracing signals

 

Redesign using a State Table

State Table for Binary Counter (Table 12-2)

Present State			Next State			Flip - Flop Inputs		
C	B	A	C^+	B^+	A^+	T_C	T_B	T_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

Redesign using a State Table

- ◆ How to create the table in the previous slide?

- ❖ If A and A+ differs, the status of Flip-Flop A is changed. So, $T_A=1$.

Variable B and C are calculated from similar way of A

- ◆ Make a K-map from a state table : Fig 12-14(below)

- ◆ Derive F/F input equations

- ❖ $T_C=AB$, $T_B=A$, $T_A=1$


- ◆ same result as previous

		C	
		0	1
BA	00	0	0
	01	0	0
	11	1	1
	10	0	0
		T_C	



		C	
		0	1
BA	00	0	0
	01	1	1
	11	1	1
	10	0	0
		T_B	

Design of Binary Counters

 Binary Counter with D Flip-Flops using conversion of D to T (Fig 11-24(b))



(b) Conversion of D to T

  


Redesign of Binary Counter

The D input equations derived from the maps are

$$D_A = A^+ = A'$$

$$D_B = B^+ = BA' + B'A = B \oplus A$$


$$D_C = C^+ = C'BA + CB' + CA' = C'BA + C(BA)' = C \oplus BA$$

- ◆ Compare the above results with Figure 12-15
- ◆ Same Diagram?
- ◆ why??  A xor 1 = A'

Counters for Other Sequences

The sequence of states of a counter is not in straight binary order.

State Graph for Counter
(Figure 12-21)

 

State Table for Figure 21.21
(Table 12-3)

C	B	A	C ⁺	B ⁺	A ⁺
0	0	0	1	0	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	0	0	0
1	0	0	1	1	1
1	0	1	-	-	-
1	1	0	-	-	-
1	1	1	0	1	0

Counters for Other Sequences

◆ State graph

- ❖ 임의의 순서를 나타냄


◆ State table

- ❖ note : unspecified next state
- ❖ 이전 예제처럼 state table을 완성하거나(as in Table 12-2)
- ❖ next-state map을 먼저 plot한 후 이 map으로부터 T_A , T_B , T_C 유도
 - ❖ 편리한 방법


Counters for Other Sequences

The next-state maps in Figure 12-22(a) are easily plotted from inspection of Table 12-3 → **Use T-F/F**

Figure 12-22

 

(a) Next-state maps for Table 12-3

 

(b) Derivation of T inputs

Counters for Other Sequences


- ◆ make next state maps – how?
- ◆ derive T input maps from next-state map
- ◆ $T=1$ whenever Q^+ is different from Q
- ◆ From the below table
 - $T=Q^+$ when $Q=0$
 - $T=(Q^+)'$ when $Q=1$
- ◆ Therefore, Copy $Q=0$ half, complement $Q=1$ half

Q	Q^+	T
0	0	0
0	1	1
1	0	1
1	1	0

$T = Q^+ \oplus Q$

Counters for Other Sequences

 
**Counter Using
T Flip-Flops
(Figure 12-23)**



Timing Diagram for Figure 12-23 (Figure 12-24)

P						
C	0	1	1	0	0	0
B	0	0	1	1	1	0
A	0	0	1	0	1	0
T_C						
T_B						
T_A						

Figure 12-23

 


State Graph for Counter

(Figure 12-25)

C=0, B=0, A=1 인경우

Tc=Tb=1, Ta=0

=>From Fig. 12-23

 

Counters for Other Sequences

Procedure to design a counter using T F/F's:

1. Form a state table which gives the next F/F states for each combination of present F/F states.
2. Plot the next-state maps from the table.
3. Plot a T input map for each F/F .
4. Find the T input equations from the maps and realize the circuit.

Counter Design using D F/F

- ◆ Counting sequence : same as in Fig 12-21
- ◆ $Q^+ = D \rightarrow$ D input map is identical with next-state map
- ◆ $D_C = C^+ = B'$
 $D_B = B^+ = C + BA'$
 $D_A = A^+ = CA' + BA' = A'(C + B)$
- ◆ Result : Fig 12-26

Fig 12-21


 


Fig 12-26



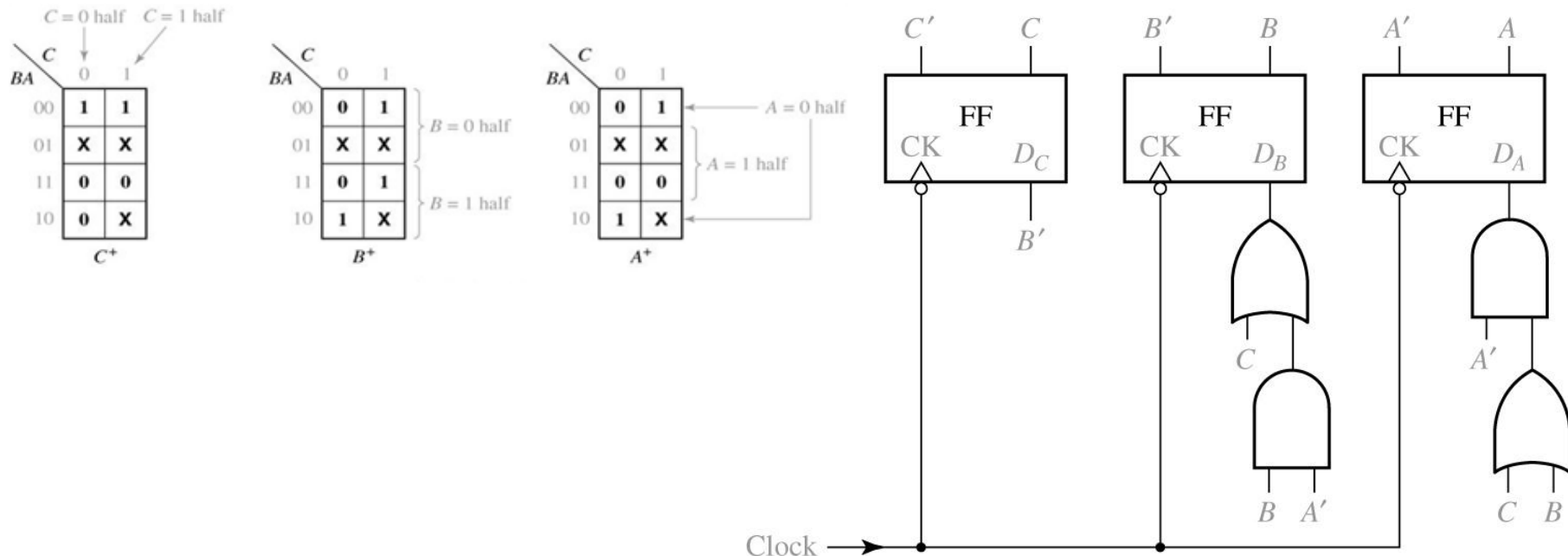


Redesign Binary Counter Using D F/F's

- ◆ 1st method : by converting F/F's → Result Fig 12-15
- ◆ 2nd method:
 - ❖ State table (Table 12-2)
 - ❖ Next state maps
 - ❖ Flip-flop input maps
 - ❖ Flip-flop input equations
- ◆ For D flip-flops,
next state map = flip-flop input map (since $Q^+ = D$)

Karnaugh Maps for D Flip-Flops from Table 12-2 (Figure 12-16)

Present State			Next State			Flip - Flop Inputs		
C	B	A	C^+	B^+	A^+	T_C	T_B	T_A
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

   

Counter Design using S-R and J-K F/Fs

S-R Flip-Flop Inputs (Table 12-5)

S	R	Q	Q^+	Q	Q^+	S	R	Q	Q^+	S	R
0	0	0	0	0	0	{	0	0	0	0	×
0	0	1	1				0	1	0	1	0
0	1	0	0	0	1		1	0	1	0	1
0	1	1	0	1	0		0	1	1	1	×
1	0	0	1	1	1	{	0	0			
1	0	1	1				1	0			
1	1	0	-								
1	1	1	-								

(a) (b) (c)

Inputs not
allowed

Counter Design Using S-R F/Fs

With columns added for the S and R flip-flop inputs (Table 12-6)

												Q	Q^+	S	R
												0	0	0	×
												0	1	1	0
												1	0	0	1
												1	1	×	0
C	B	A	C^+	B^+	A^+	S_C	R_C	S_B	R_B	S_A	R_A				
0	0	0	1	0	0	1	0	0	×	0	×				
0	0	1	-	-	-	×	×	×	×	×	×				
0	1	0	0	1	1	0	×	×	0	1	0				
0	1	1	0	0	0	0	×	0	1	0	1				
1	0	0	1	1	1	×	0	1	0	1	0				
1	0	1	-	-	-	×	×	×	×	×	×				
1	1	0	-	-	-	×	×	×	×	×	×				
1	1	1	0	1	0	0	1	×	0	0	1				


Counter Design using S-R Flip-Flops

◆ S


- ❖ Q=0 half : copy
- ❖ Q=1 half : replace 1 with X

◆ R

 
- ❖ Q=0 half : replace 0 with X, fill 0
- ❖ Q=1 half : complement



(a) Next-state maps

 

(b) S-R flip-flop equations

 

(c) Logic circuit

Counter Design Using J-K Flip-Flops

J-K Flip-Flop Inputs (Table 12-7)

J	K	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(a)

Q	Q^+	J	K
0	0	{	0
			0
0	1	{	1
			1
1	0	{	0
			1
1	1	{	0
			1

(b)

Q	Q^+	J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0

(c)

Counter Design using J-K Flip-Flops

With columns added for the J and K flip-flop inputs (Table 12-8)

C	B	A	C^+	B^+	A^+	J_C	K_C	J_B	K_B	J_A	K_A
0	0	0	1	0	0	1	×	0	×	0	×
0	0	1	-	-	-	×	×	×	×	×	×
0	1	0	0	1	1	0	×	×	0	1	×
0	1	1	0	0	0	0	×	×	1	×	1
1	0	0	1	1	1	×	0	1	×	1	×
1	0	1	-	-	-	×	×	×	×	×	×
1	1	0	-	-	-	×	×	×	×	×	×
1	1	1	0	1	0	×	1	×	0	×	1

Q	Q^+	J	K
0	0	0	×
0	1	1	×
1	0	×	1
1	1	×	0


Counter Design using J-K Flip-Flops

◆ J


- ❖ Q=0 half : copy
- ❖ Q=1 half : X

◆ K

 - ❖ Q=0 half : X
- ❖ Q=1 half : complement




(a) Next-state maps

 

 (b) J-K flip-flop input equations

**Counter of Figure 12-21
Using J-K Flip-Flops
(Figure 12-28)**



(c) Logic circuit (omitting the feedback lines)

Derivation of Flip-Flop Input Equations–Summary

Determination of Flip-Flop Input Equations from Next-State Equations Using Karnaugh Maps (Table 12-9)

Type of Flip-Flop	Input	$Q = 0$		$Q = 1$		Rules for Forming Input Map From Next-State Map*	
		$Q^+ = 0$	$Q^+ = 1$	$Q^+ = 0$	$Q^+ = 1$	$Q = 0$ Half of Map	$Q = 1$ Half of Map
Delay	D	0	1	0	1	no change	no change
Trigger	T	0	1	1	0	no change	complement
Set-Reset	S	0	1	0	X	no change	replace 1's with X's**
	R	X	0	1	0	replace 0's with X's**	complement
J-K	J	0	1	X	X	no change	fill in with X's
	K	X	X	1	0	fill in with X's	complement

Q^+ means the next state of Q

X is a don't care

*Always copy X's from the next-state map onto the input maps first.

**Fill in the remaining squares with 0's.

Q	Q^+	S	R	Q	Q^+	J	K
0	0	0	x	0	0	0	x
0	1	1	0	0	1	1	x
1	0	0	1	1	0	x	1
1	1	x	0	1	1	x	0

Table 12-9

◆ T

- ❖ Q=0 half : copy
- ❖ Q=1 half : complement

◆ S

- ❖ Q=0 half : copy
- ❖ Q=1 half : replace 1 with X

◆ R

- ❖ Q=0 half : replace 0 with X, fill 0
- ❖ Q=1 half : complement

◆ J

- ❖ Q=0 half : copy
- ❖ Q=1 half : X

◆ K

- ❖ Q=0 half : X
- ❖ Q=1 half : complement

		Q	
		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	X

Q^+

Next-state map

		Q	
		0	1
AB	00	0	1
	01	1	0
	11	0	0
	10	1	X

$$D = Q'A'B + QB' + AB'$$

D input map

		Q	
		0	1
AB	00	0	0
	01	1	1
	11	0	1
	10	1	X

$$T = A'B + AB' + QB$$

T input map

		Q	
		0	1
AB	00	0	X
	01	1	0
	11	0	0
	10	1	X

$$S = AB' + Q'A'B$$

		Q	
		0	1
AB	00	X	0
	01	0	1
	11	X	1
	10	0	X

$$R = QB$$

S-R input maps

		Q	
		0	1
AB	00	0	X
	01	1	X
	11	0	X
	10	1	X

$$J = A'B + AB'$$


		Q	
		0	1
AB	00	X	0
	01	X	1
	11	X	1
	10	X	X

$$K = B$$

J-K input maps


Derivation of Flip-Flop Input Equations

 Derivation of Flip-Flop Input Equations Using 4-Variable Maps (Figure 12-29)



Analysis of Un-Down Counter

 State Graph and Table for Up-Down counter (Figure 12-17)



When $U=1$, Up counting


When $D=1$, Down counting

CBA	$C^+B^+A^+$	
	U	D
000	001	111
001	010	000
010	011	001
011	100	010
100	101	011
101	110	100
110	111	101
111	000	110

Up-Down Counter

The up-down counter can be implemented using D F/F and gate

Binary Up-Down Counter
(Figure 12-18)

 

Up-Down Counter

The corresponding logic equations are

$$D_A = A^+ = A \oplus (U + D)$$

$$D_B = B^+ = B \oplus (UA + DA')$$

$$D_C = C^+ = C \oplus (UBA + DB'A')$$

When $U=1$ and $D=0$, \rightarrow Eq (12-2)

$U=0$ and $D=1$, these equations reduce to

$$D_A = A^+ = A \oplus 1 = A' \quad (\text{A change state every clock cycle})$$


$$D_B = B^+ = B \oplus A' \quad (\text{B change state when } A = 0)$$

$$D_C = C^+ = C \oplus B'A' \quad (\text{C change state when } B = A = 0)$$

Loadable Counter

Loadable Counter with Count Enable (Figure 12-19)

Loadable counter
(Figure 12-19(a))

 


Summarizes the counter
operation
(Figure 12-19(b))

$ClrN$	Ld	Ct	C^+	B^+	A^+	
0	\times	\times	0	0	0	
1	1	\times	D_C	D_B	D_A	(load)
1	0	0	C	B	A	(no change)
1	0	1	present state + 1			

Loadable Counter

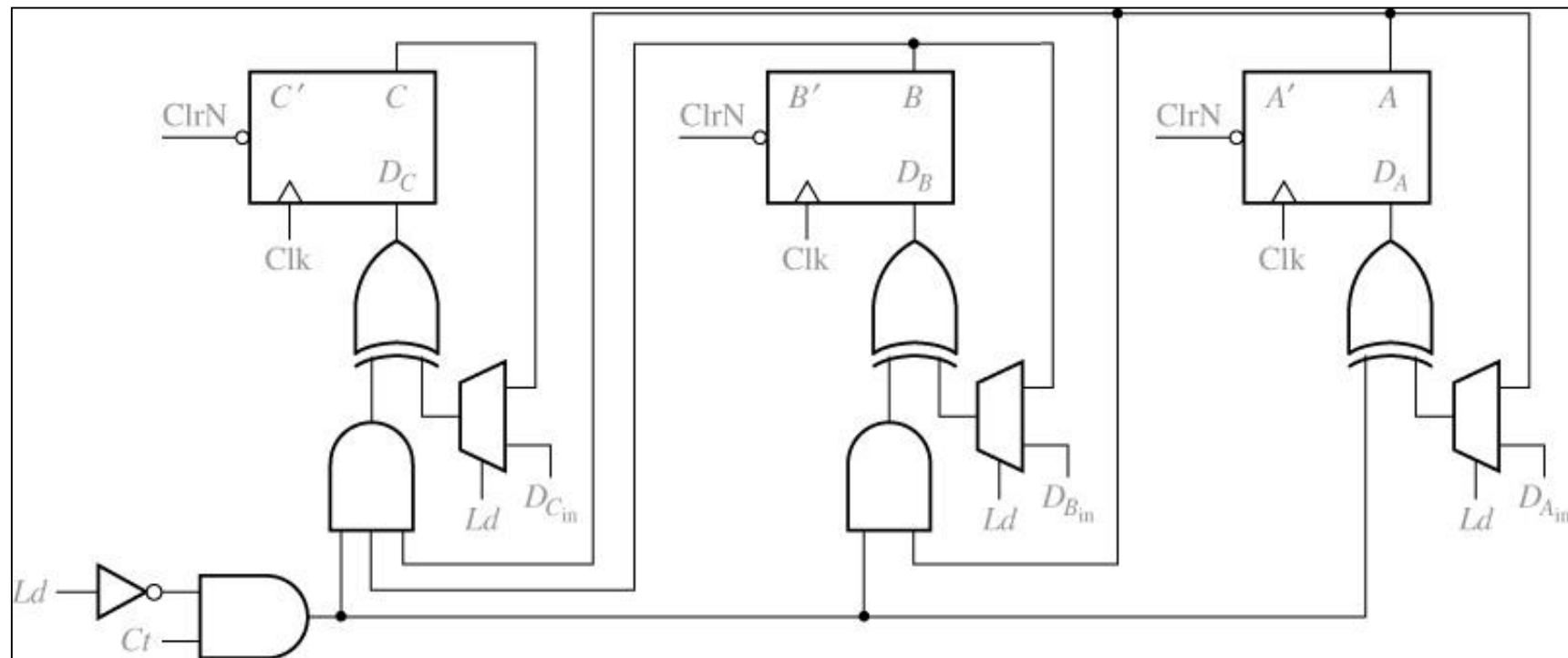- ◆ $Ld=1$
 - ❖ MUX selects D input
- ◆ $Ld=0$ & $Ct=1$
 - ❖ MUX selects one of F/F output



Design of Binary Counters

The next-state equations for the counter of Figure 12-20

$$A^+ = D_A = (Ld' \cdot A + Ld \cdot D_{Ain}) \oplus Ld' \cdot Ct$$

$$B^+ = D_B = (Ld' \cdot B + Ld \cdot D_{Bin}) \oplus Ld' \cdot Ct \cdot A$$

$$C^+ = D_C = (Ld' \cdot C + Ld \cdot D_{Cin}) \oplus Ld' \cdot Ct \cdot B \cdot A$$


Registers and Register Transfers

4-Bit D Flip-Flop Registers with Data, Load, Clear, and Clock inputs (Figure 12-1)

Grouped together D F/F
Using gated clock 12-1(a)


F/F with clock enable Figure 12-1(b)

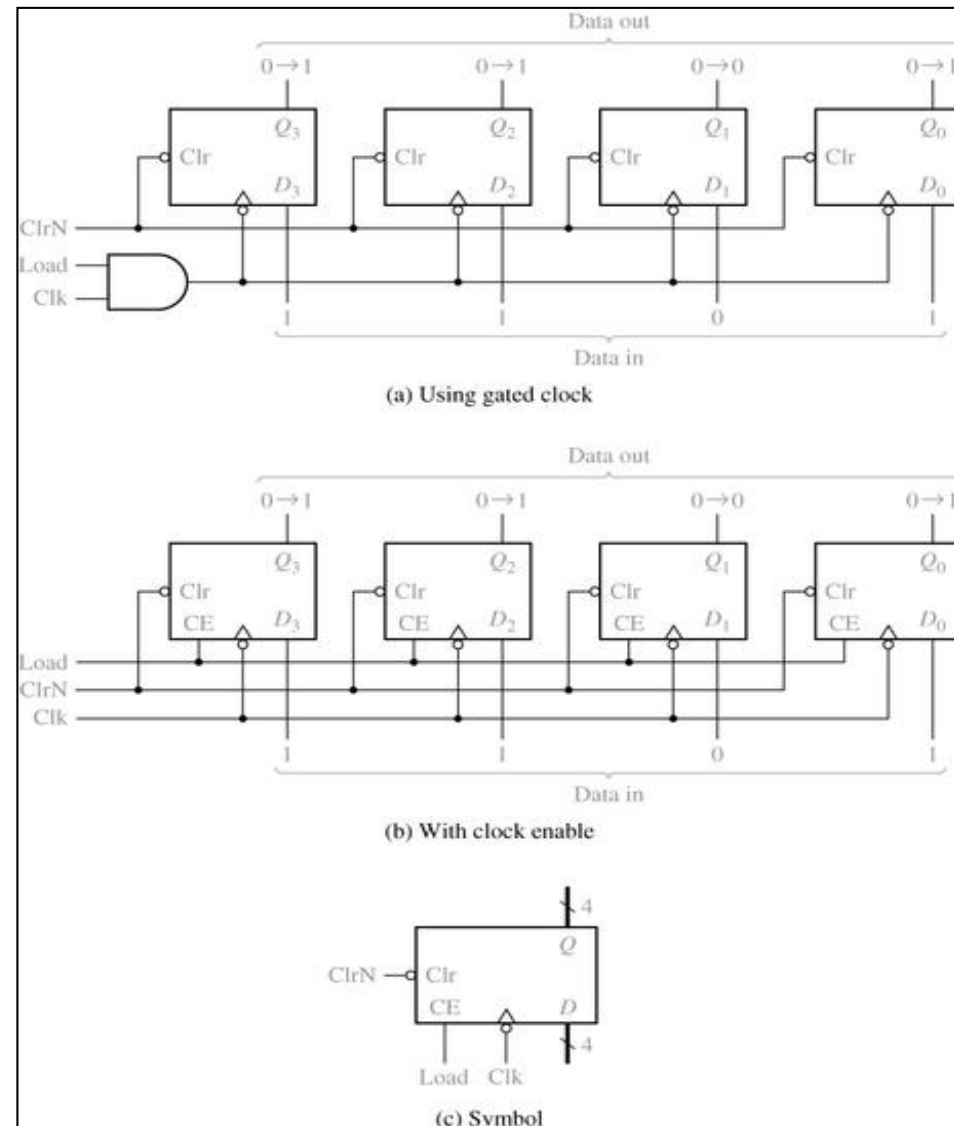Symbol for the 4-bit register using bus notation Figure 12-1(c)




Registers and Register Transfers

Data Transfer Between Registers

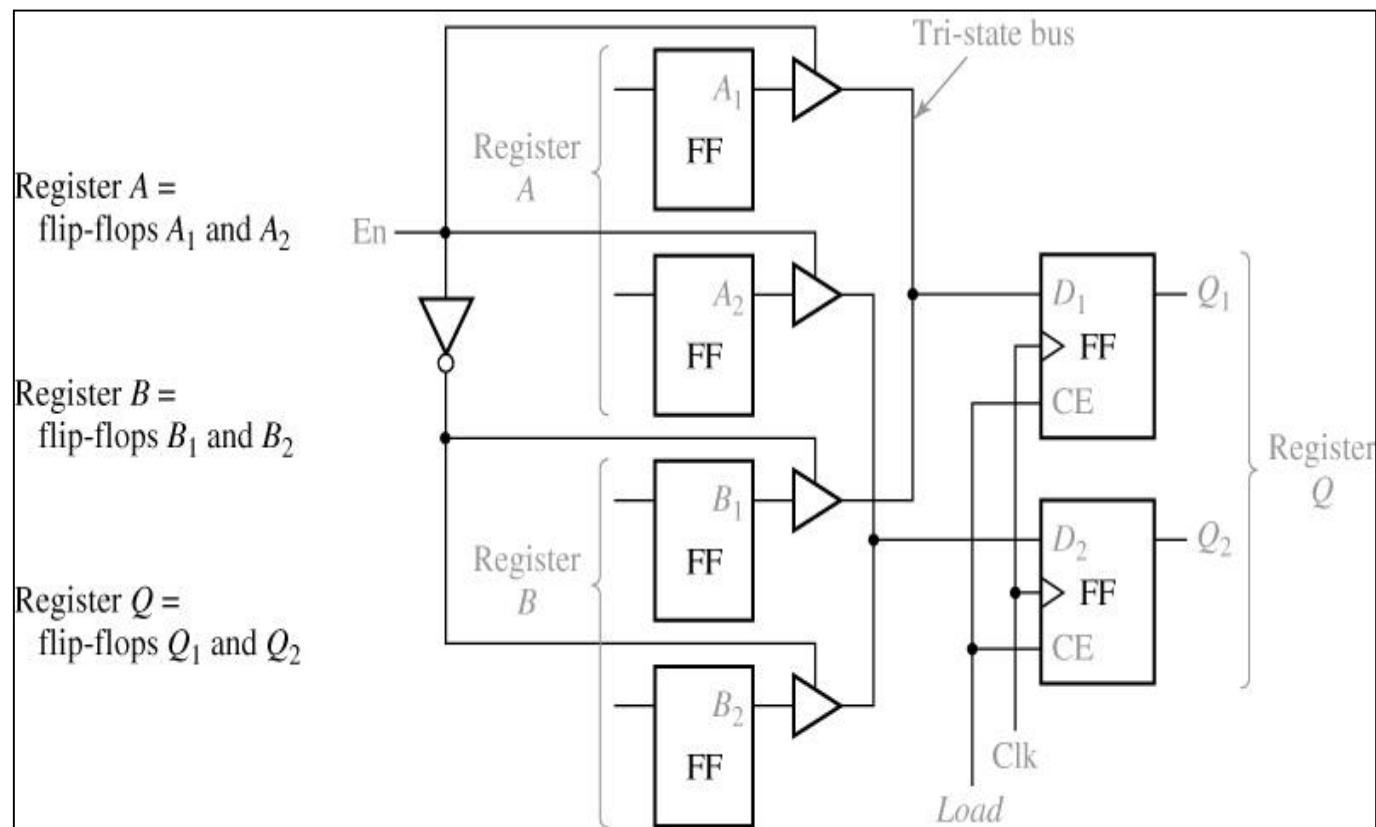


Registers and Register Transfers

 Logic Diagram for 8-Bit Register with Tri-State Output



Registers and Register Transfers

Data Transfer Using a Tri-State Bus

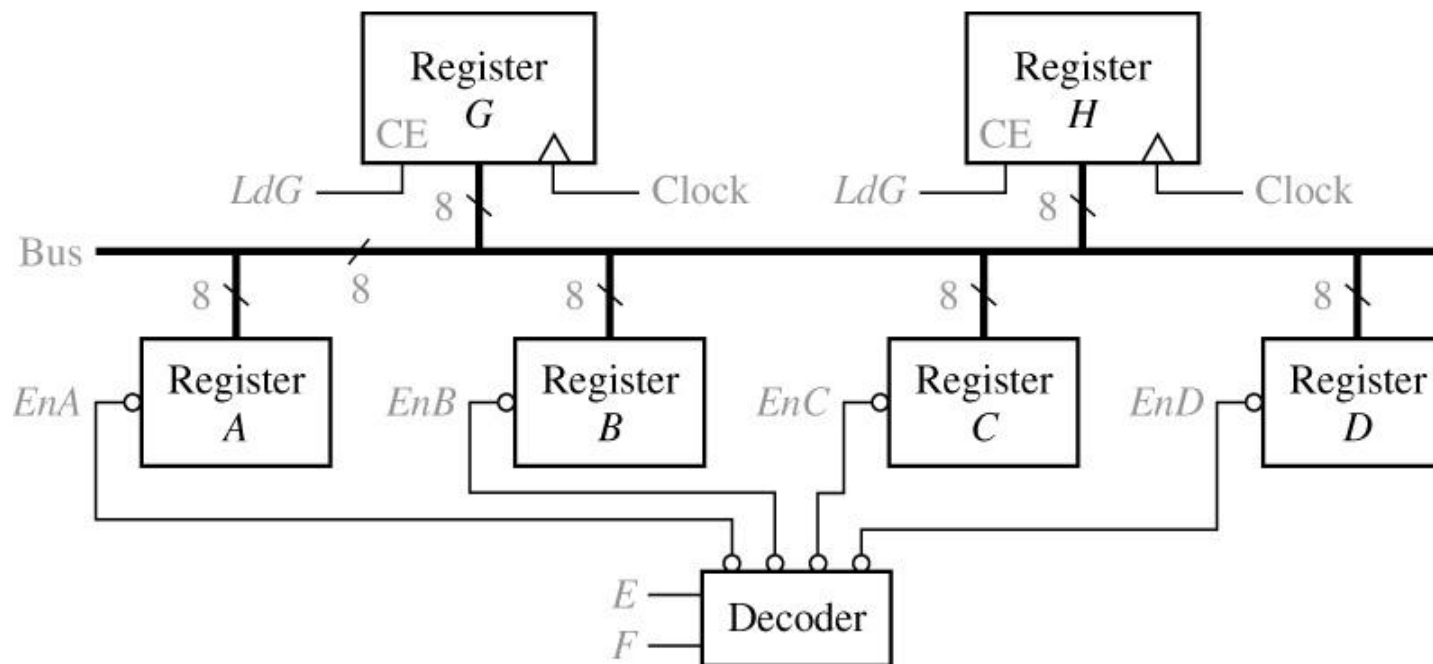

Registers and Register Transfers

How data can be transferred?

The operation can be summarized as follows:

If $EF = 00$, A is stored in G (or H).

If $EF = 01$, B is stored in G (or H).


If $EF = 10$, C is stored in G (or H).

If $EF = 11$, D is stored in G (or H).

Registers and Register Transfers


Parallel Adder with Accumulator

N-Bit Parallel Adder with Accumulator

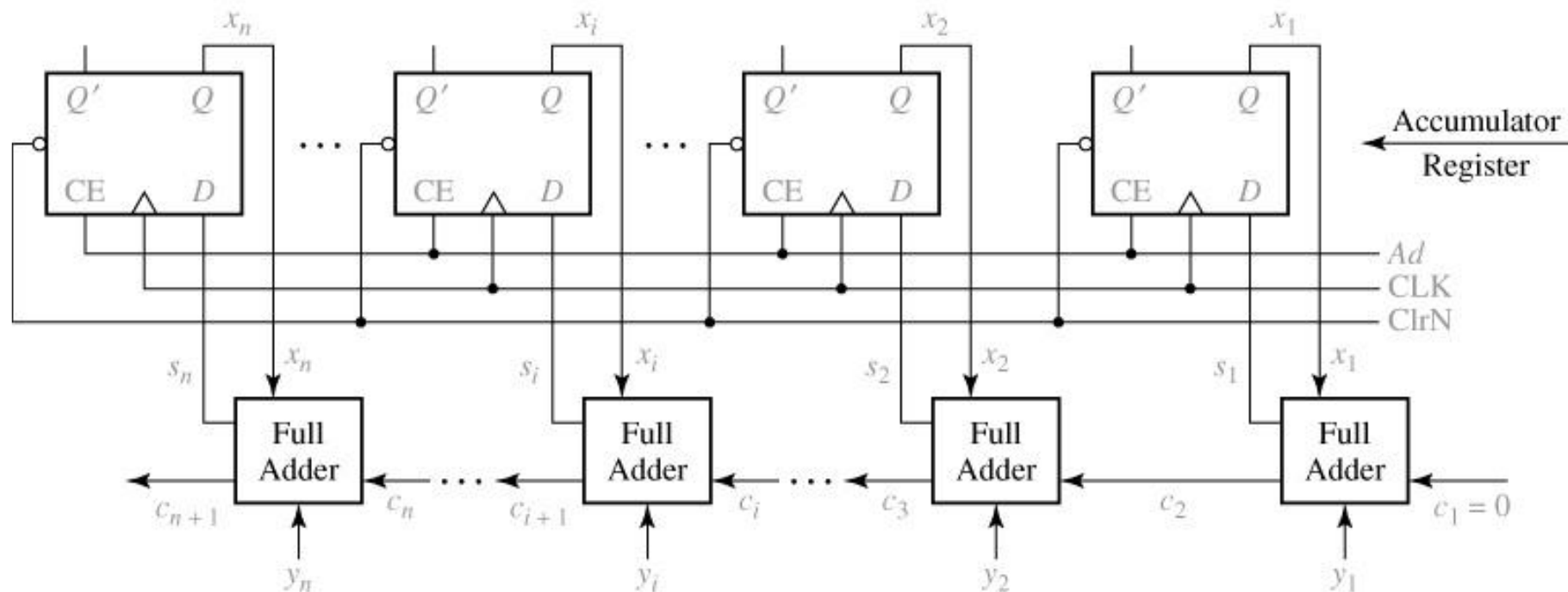


Registers and Register Transfers

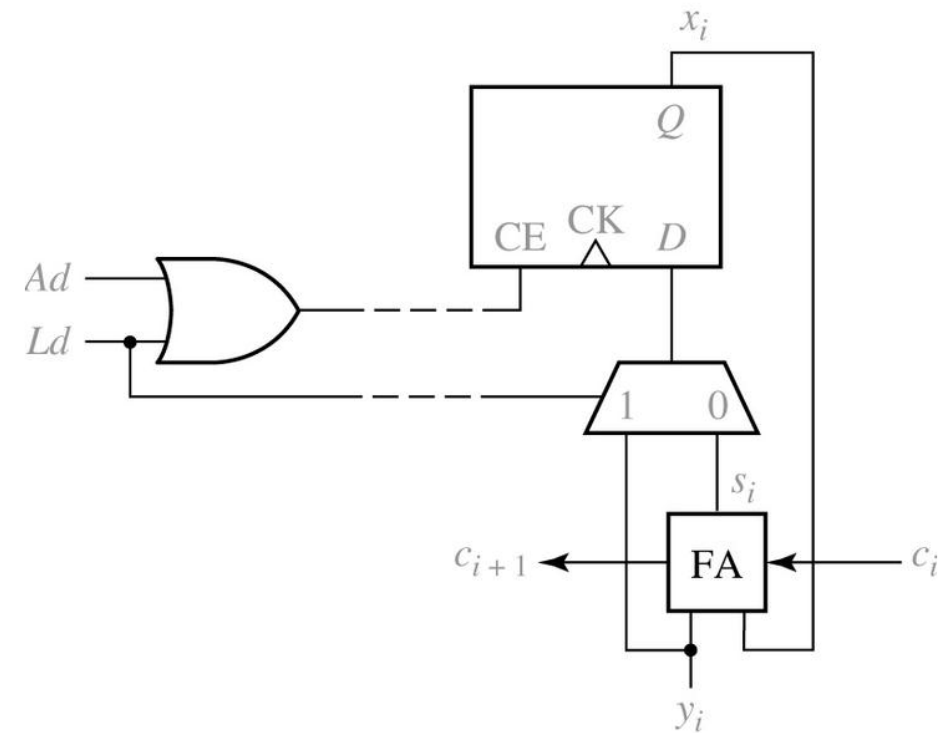Adder Cell with Multiplexer (Figure 12-6)




Shifter Registers

Right-Shift Register

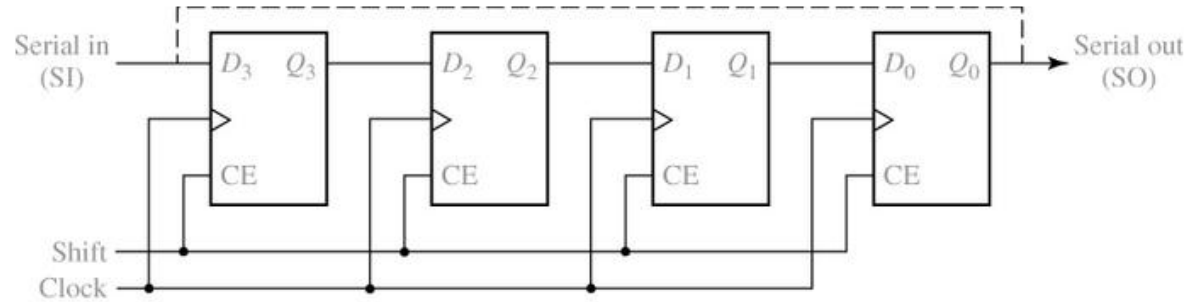


(a) Flip-flop connections

 

 
(b) Timing diagram

Shifter Registers

8-Bit Serial-in, Serial-out Shift Register




(a) Block diagram

 

 (b) Logic diagram


Shifter Registers

Typical Timing Diagram for Shift Register




Shifter Registers

 Parallel-in, Parallel-Out Right Shift Register



(a) Block diagram

 

(b) Implementation using flip-flops and MUXes

Shifter Registers

Shift Register Operation (Table 12-1)

Input		Next State				Action
$Sh(\text{Shift})$	$L(\text{Load})$	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	0	Q_3	Q_2	Q_1	Q_0	no change
0	1	D_3	D_2	D_1	D_0	load
1	\times	SI	Q_3	Q_2	Q_1	right shift

Shifter Registers

Input		Next State				Action
$Sh(\text{Shift})$	$L(\text{Load})$	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	0	Q_3	Q_2	Q_1	Q_0	no change
0	1	D_3	D_2	D_1	D_0	load
1	\times	SI	Q_3	Q_2	Q_1	right shift

The Next-state equations for the F/F are

$$Q_3^+ = Sh' \cdot L' \cdot Q_3 + Sh' \cdot L \cdot D_3 + Sh \cdot SI$$


$$Q_2^+ = Sh' \cdot L' \cdot Q_2 + Sh' \cdot L \cdot D_2 + Sh \cdot Q_3$$

$$Q_1^+ = Sh' \cdot L' \cdot Q_1 + Sh' \cdot L \cdot D_1 + Sh \cdot Q_2$$

$$Q_0^+ = Sh' \cdot L' \cdot Q_0 + Sh' \cdot L \cdot D_0 + Sh \cdot Q_1$$


Shifter Registers

Timing Diagram for Shift Register

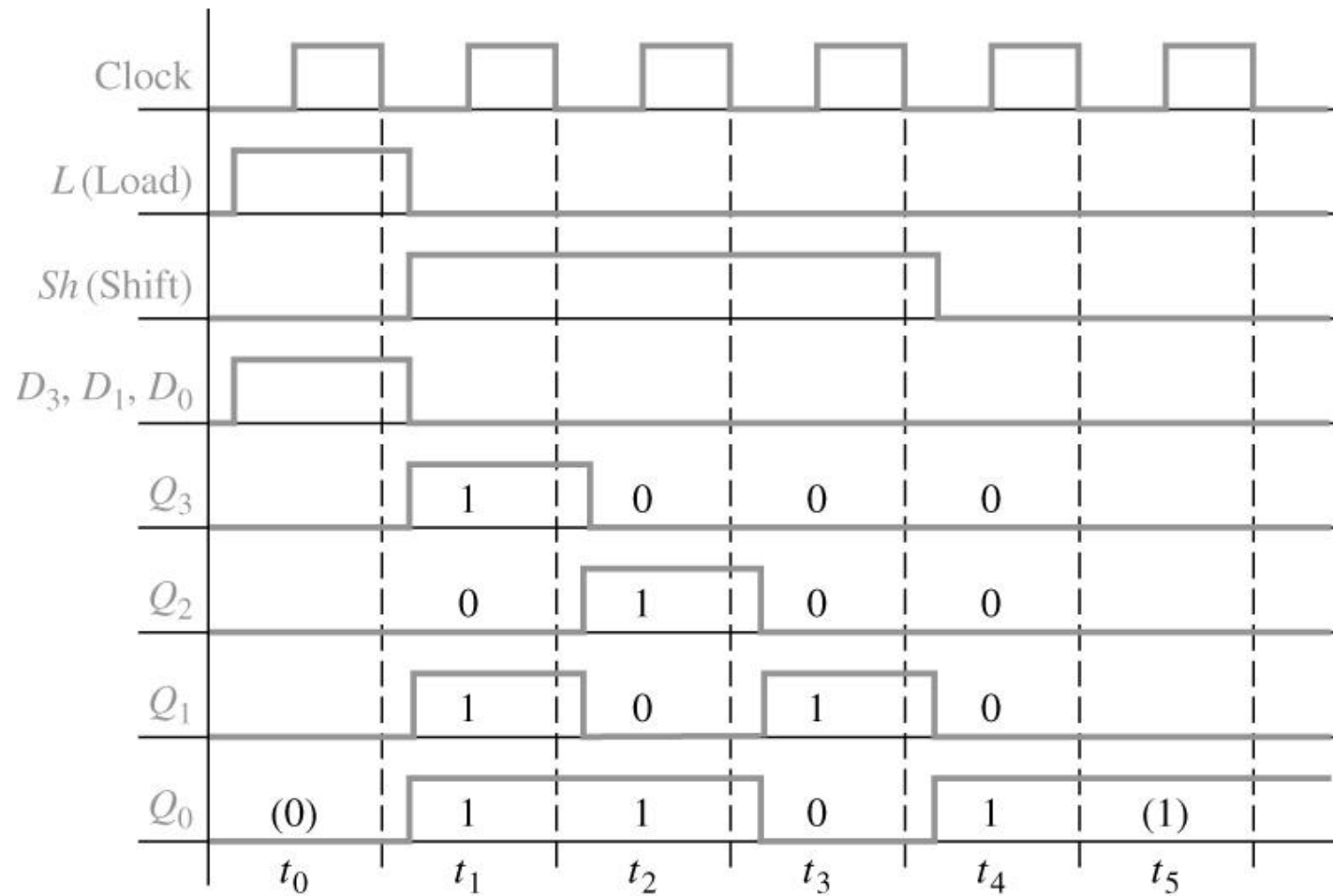


Shifter Registers

 Shift Register with Inverted Feedback (Figure 12-12) → *Johnson Counter*



(a) Flip-flop connections

 

(b) State graph

A 3-bit shift register 12-12(a)

Successive states 12-12(b)

. 000 => 100 => 110 => 111 => 011 => 001 => 000 ...
. 010 => 101 => 010 => 101