

Unit 11. Latches and Flip-Flops

Spring 2015

School of Electrical Engineering

Prof. Jong-Myon Kim

Objectives – To Learn

- ⇒ Explain in words the operation of S-R and gated D latches
- ⇒ Explain in words the operation of D, D-CE, S-R, J-K, and T flip-flops
- ⇒ Make a table and derive the characteristic (next-state) equation for such latches and flip-flops. State any necessary restrictions on the input signals
- ⇒ Draw a timing diagram relating the input and output of such latches flip-flops
- ⇒ Show how latches and flip-flops can be constructed using gates. Analyze the operation of a flip-flop that is constructed of gates and latches

Introduction

◆ Sequential switching networks

- ❖ Output depends on both present inputs and past sequence of inputs
- ❖ Latches & Flip-Flops are most commonly used memory devices

◆ Latches & Flip-Flops

- ❖ Assume one of two stable output states
- ❖ Has one or more inputs which can cause the output state to change
- ❖ Latch : a memory element that has no clock input
- ❖ Flip-Flop : a memory device that changes output state in response to a clock input and not in response to a data input


Feedback

◆ Feedback


- ❖ output of one gate is connected back into the another gate's input so as to form a closed loop
- ❖ needed to construct a switching circuit which has a memory

◆ Inverter with feedback

 - ❖ oscillate back and forth between 0 and 1
- ❖ never reach a stable condition
- ❖ oscillation rate is determined by the inverter's propagation delay



(a) Inverter with feedback

 


(b) Oscillation at inverter output

Introduction


Two inverters with feedback
two stable conditions –
stable states

Fig 11-2.

→ Stable state

 

(a)

 





(b)

Set-Reset Latch (S-R Latch)

◆ can make a simple Latch by using a feedback


◆ Operations :

    - ❖ $S=R=0, Q=0, P=1$?
 - ◆ stable? yes
- ❖ becomes $S=1$
 - ◆ $S=1, R=0, P=0, Q=1$
- ❖ $S=0$ again. Then?
 - ◆ $P=0, Q=1$
- ❖ $R=1 - Q=0, P=1$
- ❖ $R=0$: go back to first
- ❖ Two different stable state for a given set of inputs
- ❖ $R=S=1$ 을 허용하지 않으며 항상 $P=Q'$




SR Latch : Cross-Coupled Structure

 - ◆ To emphasize the symmetry, SR latch is often drawn in cross-coupled form
- ◆ Although Q comes out of NOR gate with R input, the symbol has Q directly above S input




(a)

 

(b)


Improper S-R Latch Operation

 - What if $S=R=1$?
 - $P=Q=0$ (violate basic rule of latch operation that requires the latch outputs to be complements)
 - if S & R change back to 0, $P=Q=1$ and .. (oscillate if the gate delays are exactly equal)



Set-Reset Latch

Fig 11-7. Timing Diagram for S-R Latch

 

ϵ : response time or delay time of the latch

Table 11-1. S-R Latch Operation

S R Q^+
 0 0 Q
 0 1 0
 1 0 1
 1 1 -




$S(t)$	$R(t)$	$Q(t)$	$Q(t+\epsilon)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

} Inputs not allowed


Set-Reset Latch

Fig 11-8. Map for $Q(t+\epsilon)$

 


next-state equation(다음상태 방정식) or
characteristic equation(특성방정식)

Switch Debouncing with an S-R Latch

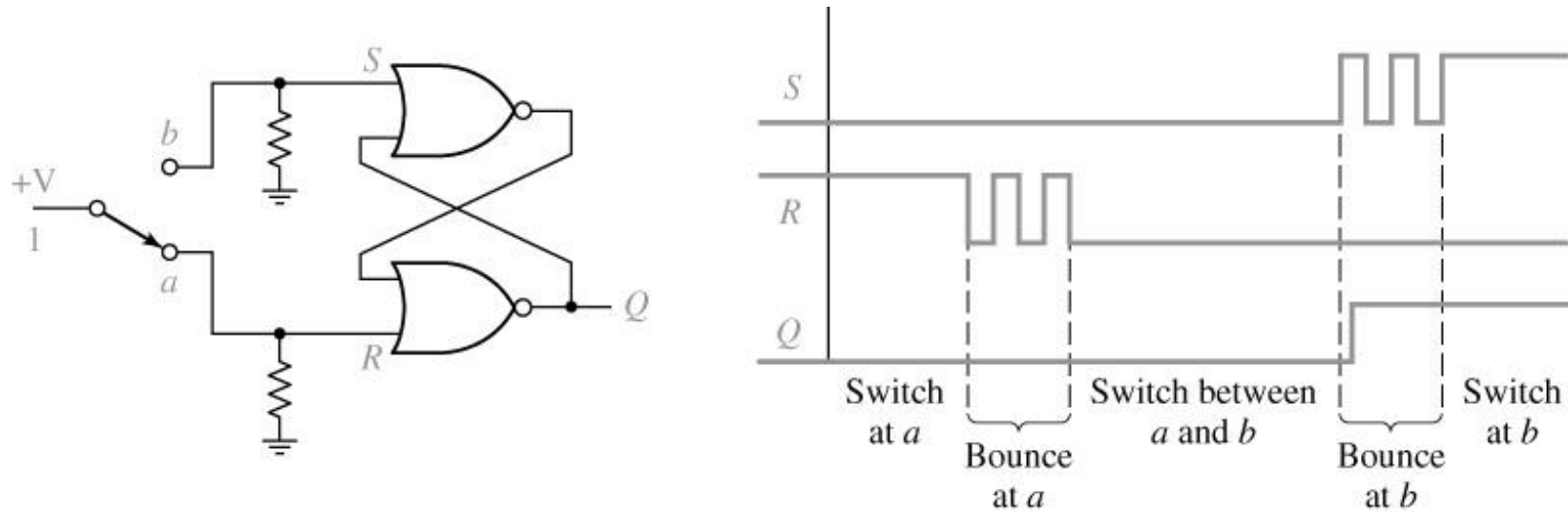


Alternative Form of Set–Reset Latch

$\overline{S} - \overline{R}$ Latch

 

(a)

 


(b)

\overline{S}	\overline{R}	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	-
0	0	1	-

} Inputs not allowed

(c)

Gated D Latch

 

- ◆ Two inputs : D, G
 - ❖ when $G=0 \rightarrow S=R=0$ \Rightarrow Q does not change
 - ❖ when $G=1, D=1, S=1, R=0$ \Rightarrow $Q=1$
 - ❖ when $G=1, D=0, S=0, R=1$ \Rightarrow $Q=0$
- ◆ \Rightarrow when $G=1$, the Q output follows D input
when $G=0$, Q does not change
- ◆ Transparent latch

Gated D Latch

Figure 11–12. Symbol and Truth Table for Gated Latch


D	Q	G	D	Q	Q^+
		0	0	0	0
		0	0	1	1
		0	1	0	0
		0	1	1	1
		1	0	0	0
		1	0	1	0
		1	1	0	1
		1	1	1	1

GD	00	01	11	10
Q				
0	0	0	1	0
1	1	1	1	0


$Q^+ = G'Q + GD$

Edge-Triggered D Flip-Flop

Figure 11-13. D Flip-Flops

 

(a) Rising-edge trigger

 


(b) Falling-edge trigger

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1


(c) Truth table

$$Q^+ = D$$


Figure 11-14. Timing for D Flip-Flop (Falling-Edge Trigger)

 

Rising-Edge-Triggered D F/F

 

 (a) Construction from two gated D latches



(b) Time analysis

◆ CLK=0, G1=1


- ❖ P output follows D input
- ❖ since G2=0, 2nd latch hold current Q

◆ CLK=1, G1=0

- ❖ current D is stored in 1st latch
- ❖ since G2=1, P flows thru 2nd latch to Q output


Edge-Triggered D Flip-Flop

Figure 11-16. Setup and Hold Times for an Edge-Triggered D Flip-Flop

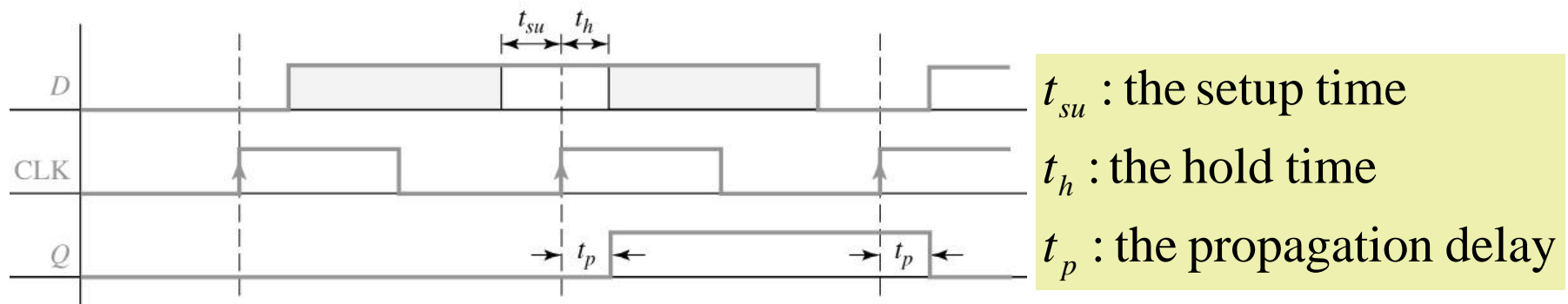


Edge-Triggered D Flip-Flop


Figure 11-17. Determination of Minimum Clock Period

 


(a) Simple flip-flop circuit

 

(b) Setup time not satisfied

 


(c) Setup time satisfied

 

(d) Minimum clock period

S-R Flip-Flop


Figure 11-18. S-R Flip-Flop

 


Operation summary :

$S=R=0$	No state change
$S=1, R=0$	Set Q to 1 (after active Ck edge)
$S=0, R=1$	Reset Q to 0 (after active Ck edge)
$S=R=1$	Not allowed

S-R F/F Implementation & Timing

 

(a) Implementation with two latches

 


(b) Timing analysis

- ◆ constructed from two S-R latches & gates
- ◆ master-slave F/F
- ◆ ML : master latch, SL : slave latch
- ◆ CLK=0
 - ❖ ML's output : appropriate value
 - ❖ SL hold prev. value Q ($S_2=R_2=0$)
- ◆ CLK 0 → 1
 - ❖ ML's P output is transferred to SL
- ◆ CLK=1
 - ❖ ML holds P
 - ❖ Q does not change
- ◆ CLK 1 → 0
 - ❖ Q(P?) value is latched in SL
 - ❖ ML processes new input
- ◆ Problem at t5?
 - ❖ → S & R inputs to change while the clock is high

J-K Flip-Flop

Figure 11-20. J-K Flip-Flop (Q Changes on the Rising Edge)

 


(a) J-K flip-flop

J	K	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q$$

 
(b) Truth table and characteristic equation



(c) J-K flip-flop timing


J-K Flip-Flop

Figure 11-21. Master-Slave J-K Flip-Flop (Q Changes on Rising Edge)

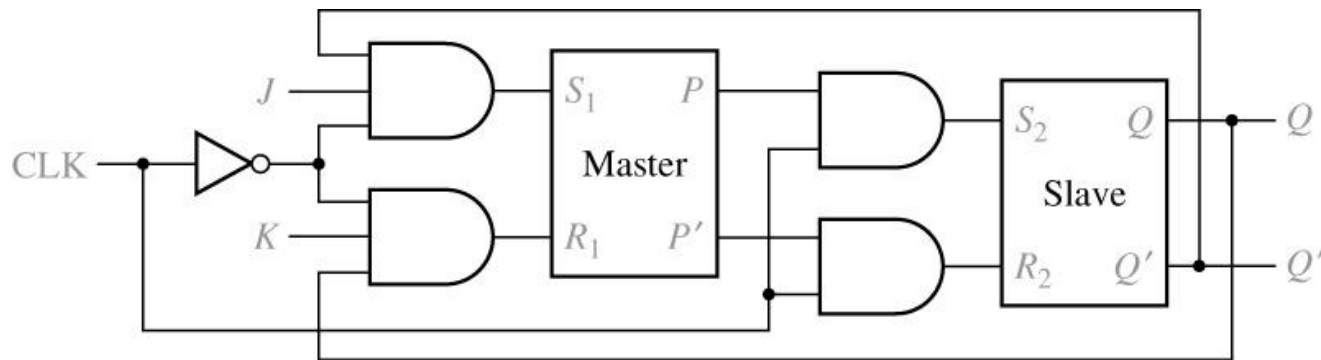

T Flip-Flop

Figure 11-22. T Flip-Flop

 


(a)

T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

(b)


$$Q^+ = T'Q + TQ' = T \oplus Q$$

Figure 11-23. Timing Diagram for T Flip-Flop (Falling-Edge Trigger)

 


T Flip-Flop

Figure 11-24. Implementation of T Flip-Flop

 

(a) Conversion of J-K to T

 


(b) Conversion of D to T

$$Q^+ = JQ' + K'Q = TQ' + T'Q$$

$$Q^+ = D = T \oplus Q = TQ' + T'Q$$

Flip-Flops with Additional Inputs

- ◆ additional inputs to set the F/F to an initial state independent of the clock
- ◆ active-low signals 
- ◆ $\text{ClrN}=0 \rightarrow Q=0$
 $\text{PreN}=0 \rightarrow Q=1$ 로 됨
- ◆ $\text{ClrN}=\text{PreN}=1 \rightarrow$ normal operation
- ◆ ClrN , PreN override the clock & D input

Flip-Flops with Additional Inputs

Figure 11-25. D Flip-Flop with Clear and Preset



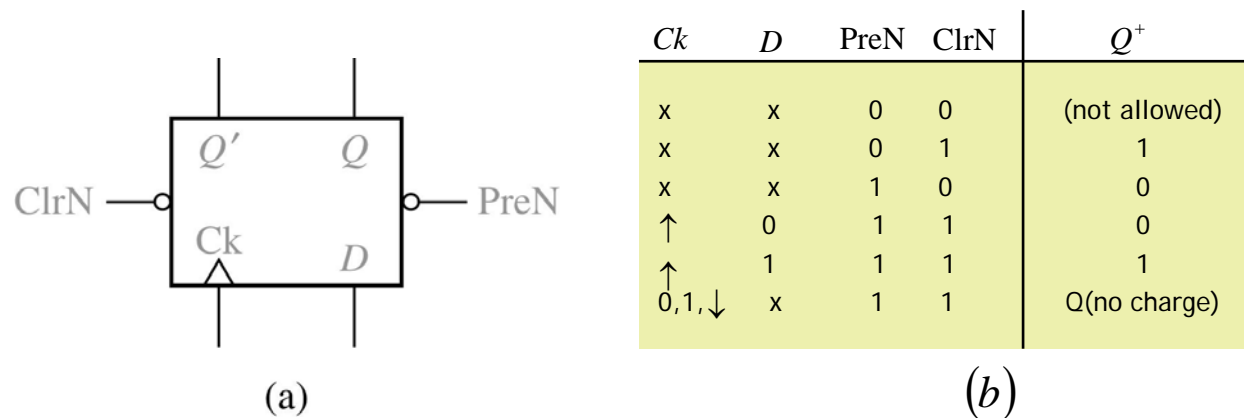


Figure 11-26. Timing Diagram for D Flip-Flop with Asynchronous Clear and Preset

 

Flip-Flops with Additional Inputs

Figure 11-27. D Flip-Flop with Clock Enable

 

The characteristic equation : $Q^+ = Q \cdot CE' + D \cdot CE$

The MUX output : $Q^+ = D = Q \cdot CE' + D_{in} \cdot CE$

Summary

$$Q^+ = S + R'Q \quad (SR = 0)$$

(S-R latch or flip-flop)

$$Q^+ = GD + G'Q$$

(gated D latch)

$$Q^+ = D$$

(D flip-flop)

$$Q^+ = D \cdot CE + Q \cdot CE'$$

(D-CE flip-flop)

$$Q^+ = JQ' + K'Q$$

(J-K flip-flop)

$$Q^+ = T \oplus Q = T'Q + TQ'$$

(T flip-flop)