

## Unit 2. Boolean Algebra

Spring 2015

School of Electrical Engineering

Prof. Jong-Myon Kim

# Objectives

---

## Topics introduced in this chapter

- ⇒ Understand the basic operations and laws of Boolean algebra
- ⇒ Relate these operations and laws to AND, OR, NOT gates and switches
- ⇒ Prove these laws using a truth table
- ⇒ Manipulation of algebraic expression using
  - ⇒ Multiplying out
  - ⇒ Factoring
  - ⇒ Simplifying
  - ⇒ Finding the complement of an expression

# Introduction

---

- ⇒ Basic mathematics for logic design: Boolean algebra
- ⇒ Restrict to switching circuits (Two state values 0, 1) – Switching algebra
- ⇒ Boolean Variable :  $X, Y, \dots$  can only have two state values (0, 1)
  - ⇒ representing True(1) False (0)

# Basic Operations


---

## ● Not (Inverter)

$$0' = 1 \text{ and } 1' = 0$$

$$X' = 1 \text{ if } X = 0 \text{ and } X' = 0 \text{ if } X = 1$$

## ● Gate Symbol

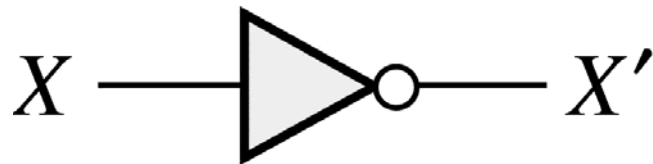

# Basic Operations


## AND

$$0 \cdot 0 = 0, 0 \cdot 1 = 0, 1 \cdot 0 = 0, 1 \cdot 1 = 1$$

## Truth Table

A	B	C = A · B
0	0	0
0	1	0
1	0	0
1	1	1

## Gate Symbol

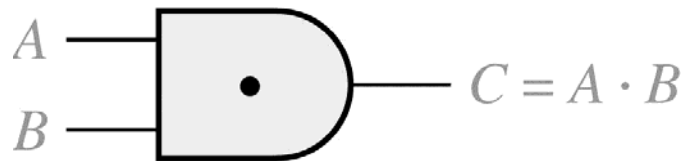

# Basic Operations


## OR

$$0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, 1 + 1 = 1$$

## Truth Table


A	B	C = A · B
0	0	0
0	1	1
1	0	1
1	1	1

## Gate Symbol

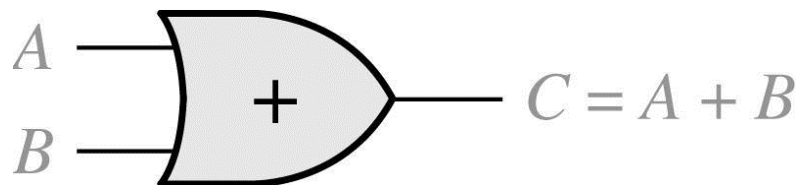


# Basic Operations


## ● Apply to Switch

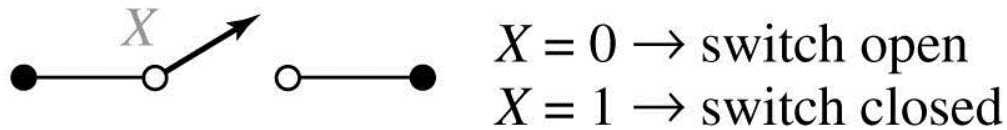

## ● AND $T=A \cdot B$

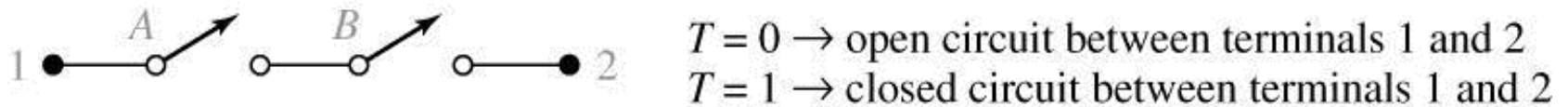

## ● OR $T=A+B$

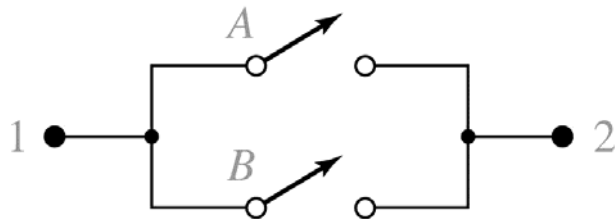


# Boolean Expressions and Truth Tables

## ● Logic Expression :

$$(AB' + C)$$

## ● Circuit of Logic

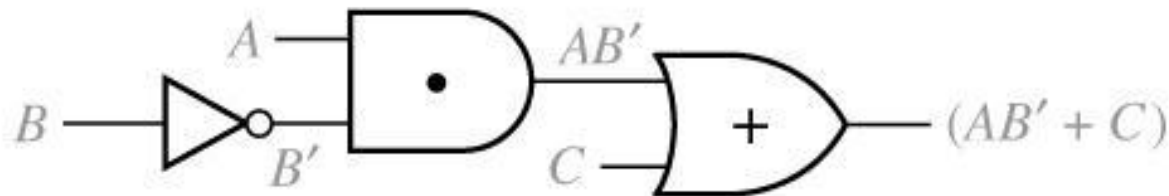




# Boolean Expressions and Truth Tables

## Logic Expression :

$$[A(C + D)]' + BE$$

## Circuit of Logic

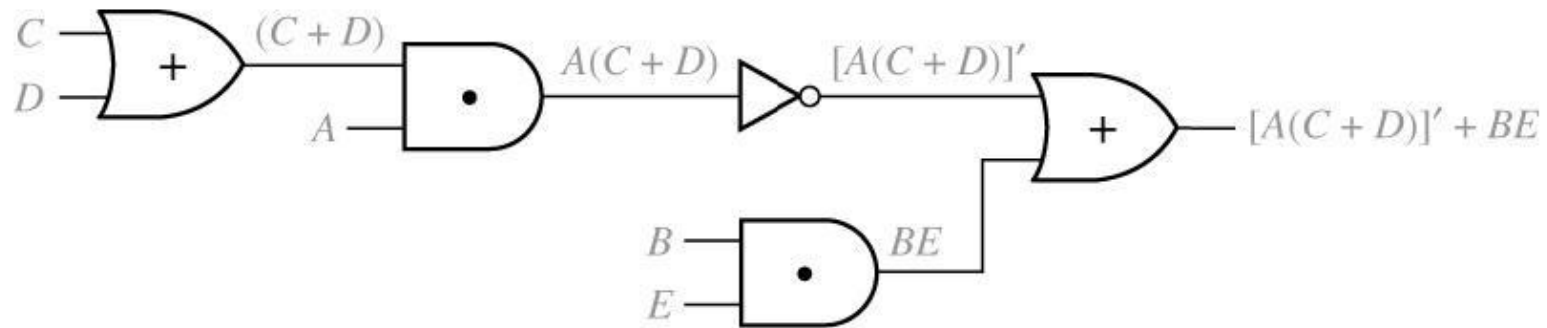


## Logic Evaluation : $A=B=C=1, D=E=0$

$$[A(C + D)]' + BE = [1(1 + 0)]' + 1 \cdot 0 = [1(1)]' + 0 = 0 + 0 = 0$$

# Boolean Expressions and Truth Tables

## 2-Input Circuit and Truth Table

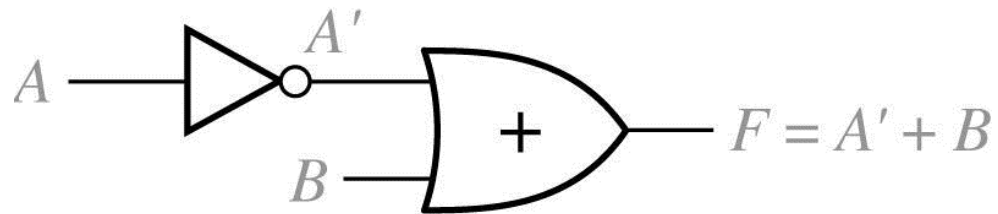

A	B	$A'$	$F = A' + B$
0	0	1	1
0	1	1	1
1	0	0	0
1	1	0	1

# Boolean Expressions and Truth Tables

## ● Proof using Truth Table

$$AB' + C = (A + C)(B' + C)$$

n variable needs  $\underbrace{2 \times 2 \times 2 \times \cdots}_{n \text{ times}} = 2^n$  rows

A B C	B'	AB'	AB' + C	A + C	B' + C	(A + C)(B' + C)
0 0 0	1	0	0	0	1	0
0 0 1	1	0	1	1	1	1
0 1 0	0	0	0	0	0	0
0 1 1	0	0	1	1	1	1
1 0 0	1	1	1	1	1	1
1 0 1	1	1	1	1	1	1
1 1 0	0	0	0	1	0	0
1 1 1	0	0	1	1	1	1

# Basic Theorems

## ■ Operations with 0, 1

$$X + 0 = X$$

$$X \cdot 1 = X$$

$$X + 1 = 1$$

$$X \cdot 0 = 0$$

## ■ Idempotent Laws

$$X + X = X$$

$$X \cdot X = X$$

## ■ Involution Laws

$$(X')' = X$$

## ■ Complementary Laws

$$X + X' = 1$$

$$X \cdot X' = 0$$



● **Proof**  $X = 0$ ,  $0 + 0' = 0 + 1$ , and if  $X = 1$ ,  $1 + 1' = 1 + 0 = 1$

## ● Examples




$$(AB' + D)E + 1 = 1$$

$$(AB' + D)(AB' + D)' = 0$$

# Basic Theorems with Switch Circuits

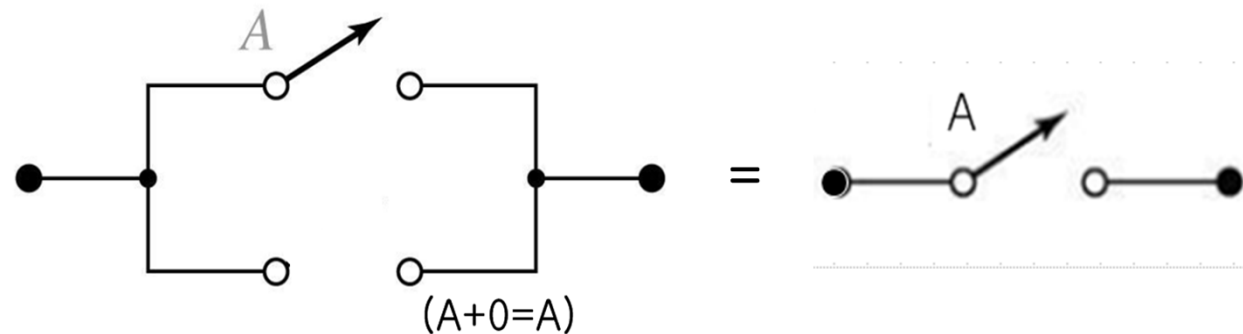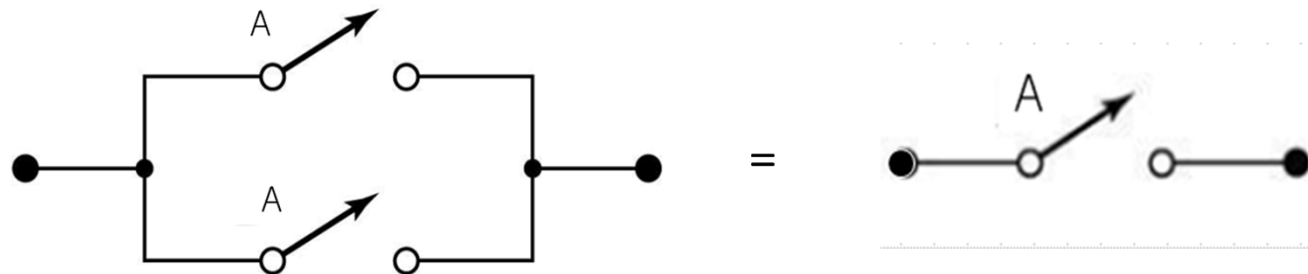

# Basic Theorems with Switch Circuits

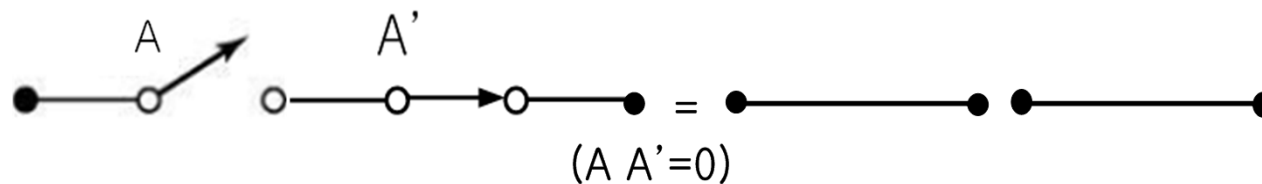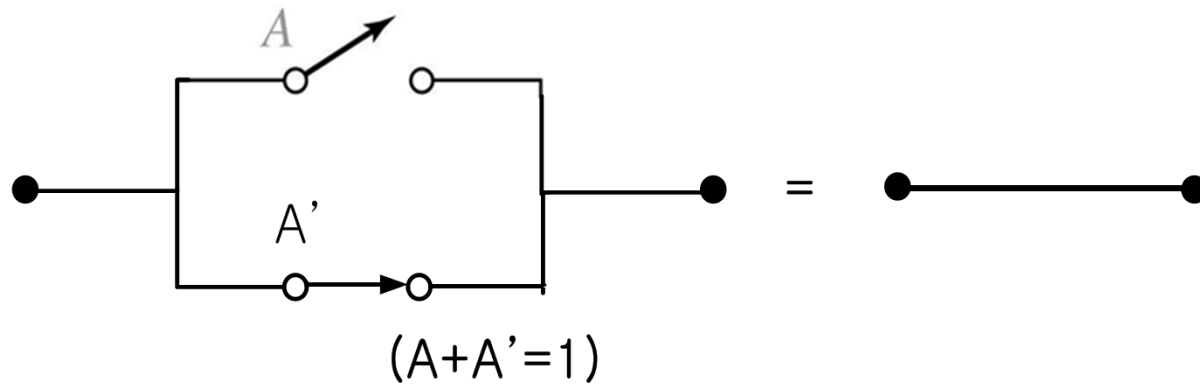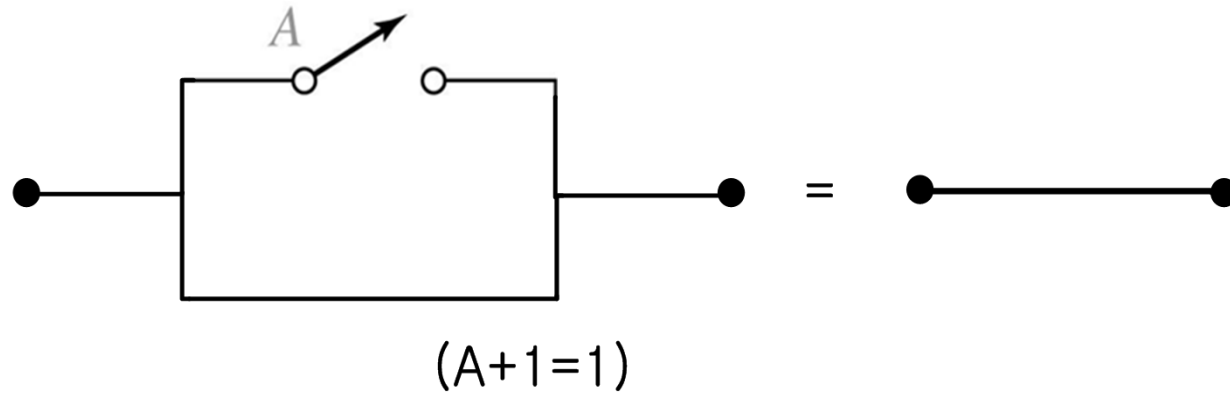

# Commutative, Associative, Distributive

■ **Commutative Laws :**  $XY = YX$ ,  $X + Y = Y + X$



■ **Associative Laws :**  $(XY)Z = X(YZ) = XYZ$

$$(X + Y) + Z = X + (Y + Z) = X + Y + Z$$

## ● **Proof of Associative Law for AND**

X Y Z	XY	YZ	(XY)Z	X(YZ)
0 0 0	0	0	0	0
0 0 1	0	0	0	0
0 1 0	0	0	0	0
0 1 1	0	1	0	0
1 0 0	0	0	0	0
1 0 1	0	0	0	0
1 1 0	1	0	0	0
1 1 1	1	1	1	1

# Associative Laws for AND and OR

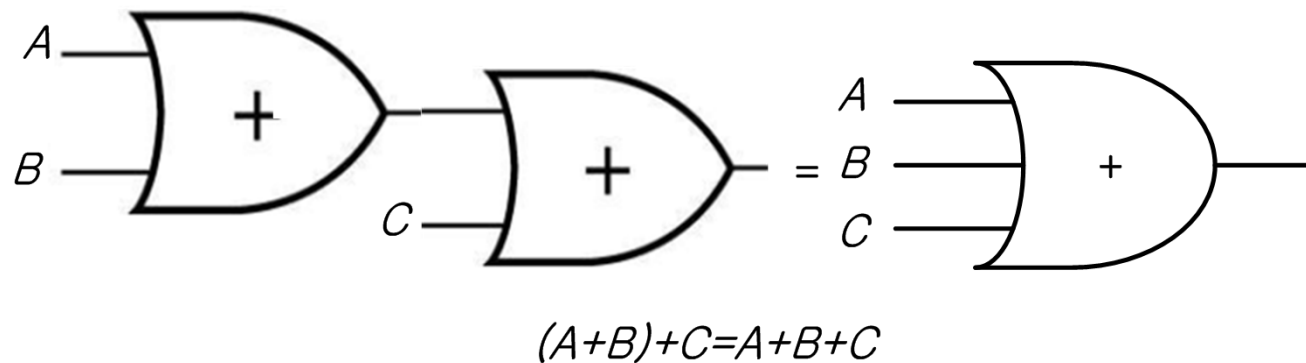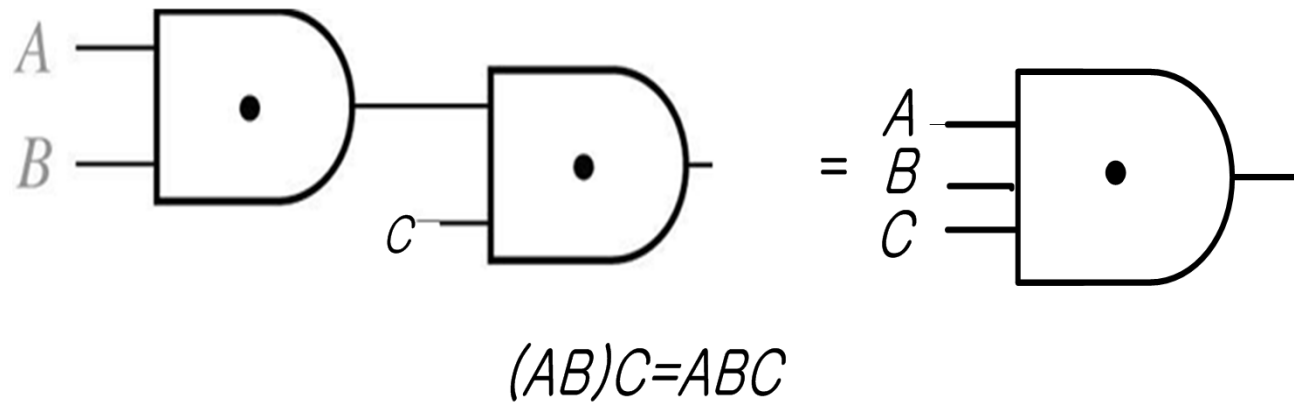



# Commutative, Associative, Distributive

■ **AND :**  $XYZ = 1$  iff  $X = Y = Z = 1$

■ **OR :**  $X + Y + Z = 0$  iff  $X = Y = Z = 0$

■ **Distribute Laws :**  $X(Y + Z) = XY + XZ$

$$X + YZ = (X + Y)(X + Z)$$

*Valid only Boolean  
algebra not for ordinary  
algebra*



## Proof

$$\begin{aligned}(X + Y)(X + Z) &= X(X + Z) + Y(X + Z) = XX + XZ + YX + YZ \\ &= X + XZ + XY + YZ = X \cdot 1 + XZ + XY + YZ \\ &= X(1 + Z + Y) + YZ = X \cdot 1 + YZ = X + YZ\end{aligned}$$

# Simplification Theorems

## ■ Useful Theorems for Simplification

$$XY + XY' = X \quad (X + Y)(X + Y') = X$$

$$X + XY = X \quad X(X + Y) = X$$

$$(X + Y')Y = XY \quad XY' + Y = X + Y$$


## ● Proof

$$X + XY = X \cdot 1 + XY = X(1 + Y) = X \cdot 1 = X$$

$$X(X + Y) = XX + XY = X + XY = X$$

$$Y + XY' = (Y + X)(Y + Y') = (Y + X)1 = Y + X$$

## ● Proof with Switch

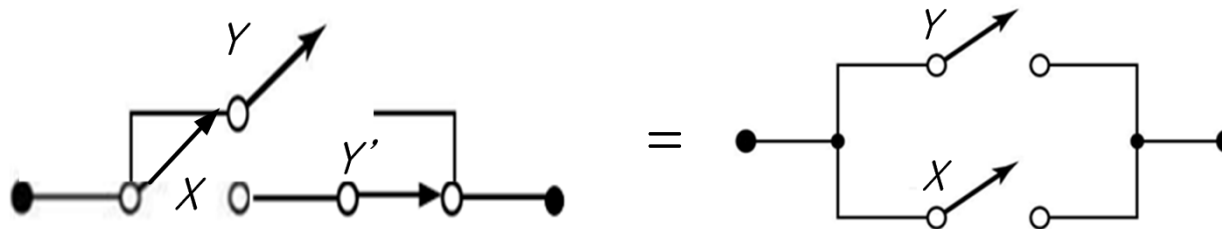


# Simplification Theorems

---

## ■ Equivalent Gate Circuits

$$F = A(A' + B) = AB$$

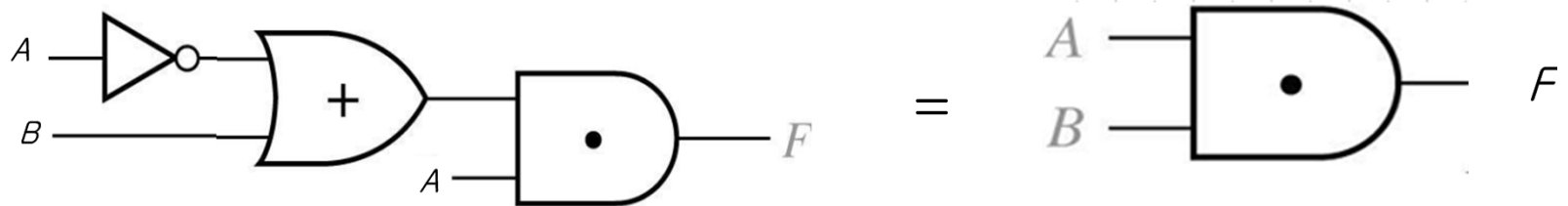

# Multiplying Out and Factoring

---

To obtain a sum-of-product form → Multiplying out using distributive laws

■ Sum of product form :  $AB' + CD'E + AC'E$

■ Not in sum of product form :  $(A + B)CD + EF$

■ Multiplying out and eliminating redundant terms :

$$\begin{aligned}(A + BC)(A + D + E) &= A + AD + AE + ABC + BCD + BCE \\ &= A(1 + D + E + BC) + BCD + BCE \\ &= A + BCD + BCE\end{aligned}$$


# Multiplying Out and Factoring

---



To obtain a product of sum form → all sums are the sum of single variable

■ Product of sum form :  $(A + B')(C + D' + E)(A + C' + E')$


# Circuits of SOP and POS Forms

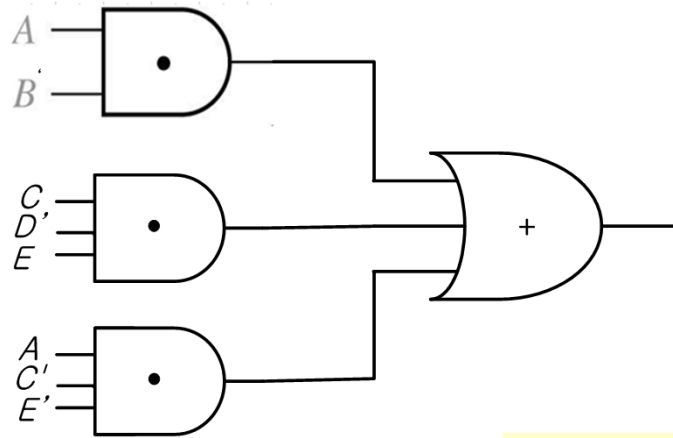

**Sum of product form**

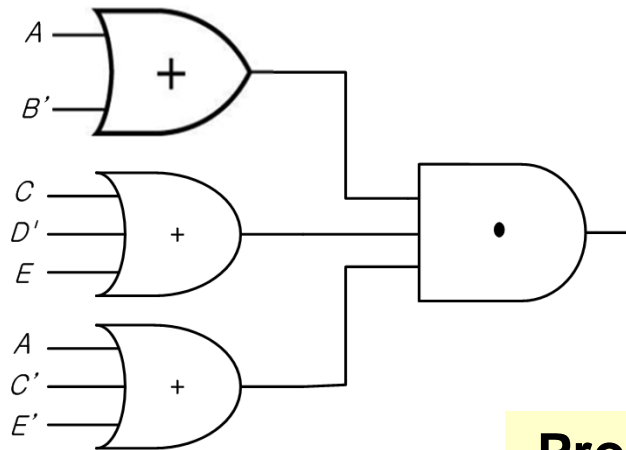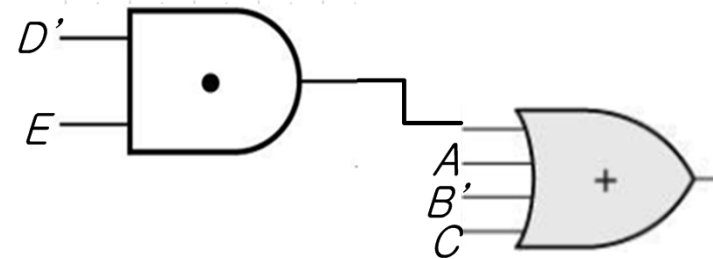

**Product of sum form**

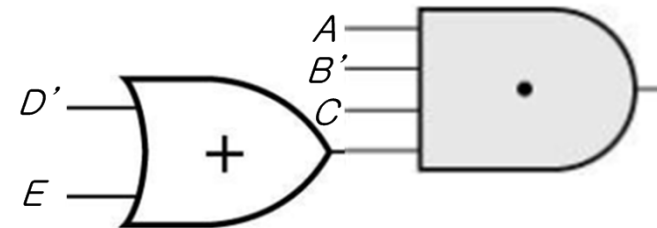

# DeMorgan's Laws

## DeMorgan's Laws

$$(X + Y)' = X'Y'$$

$$(XY)' = X' + Y'$$

## Proof

X	Y	X'Y'	X + Y	(X + Y)'	X'Y'	XY	(XY)'	X' + Y'
0	0	1	0	1	1	0	1	1
0	1	1	1	0	0	0	1	1
1	0	0	1	0	0	0	1	1
1	1	0	1	0	0	1	0	0

## DeMorgan's Laws for n variables

$$(X_1 + X_2 + X_3 + \dots + X_n)' = X_1' X_2' X_3' \dots X_n'$$

$$(X_1 X_2 X_3 \dots X_n)' = X_1' + X_2' + X_3' + \dots + X_n'$$

## Example

$$(X_1 + X_2 + X_3)' = (X_1 + X_2)' X_3' = X_1' X_2' X_3'$$

# DeMorgan's Laws

## ■ Inverse of $A'B + AB'$

$$F' = (A'B + AB')' = (A'B)'(AB')' = (A + B')(A' + B) \\ = AA' + AB + B'A' + BB' = A'B' + AB$$

A B	A' B	A B'	F = A'B + AB'	A' B'	A B	F' = A'B' + AB
0 0	0	0	0	1	0	1
0 1	1	0	1	0	0	0
1 0	0	1	1	0	0	0
1 1	0	0	0	0	1	1

## ■ Dual: 'dual' is formed by replacing AND with OR, OR with AND, 0 with 1, 1 with 0

$$(XYZ...) ^D = X + Y + Z + ... \quad (X + Y + Z + ...) ^D = XYZ...$$

$$(AB' + C)' = (AB')'C' = (A'B)C', \quad \text{so} \quad (AB' + C)^D = (A + B')C$$